


# EECS 16A      Designing Information Devices and Systems I

## Summer 2023      Discussion 2B


### 1. Circuit Components and Ohm's Law

(a) We will look at the  $I - V$  characteristics of different circuit components. For each of the components listed below, plot the  $I_{elem} - V_{elem}$  characteristic curves.


i. Wire

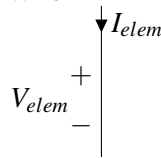


ii. Open Circuit

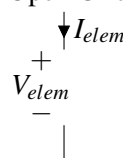


iii. Resistor

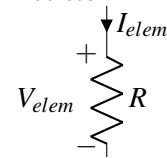

iv. Voltage Source

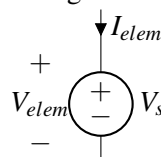


v. Current Source

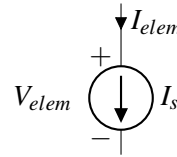


(b) Use Ohm's Law to find the missing component values in the circuits below. You may assume that each circuit is part of a larger circuit where there is a closed path for current to flow.


i.  $R = ?$

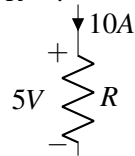


ii.  $I = ?$

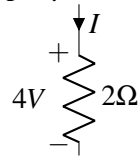

iii.  $V_R = ?$

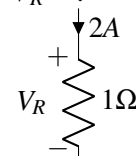


## 2. Label the Nodes

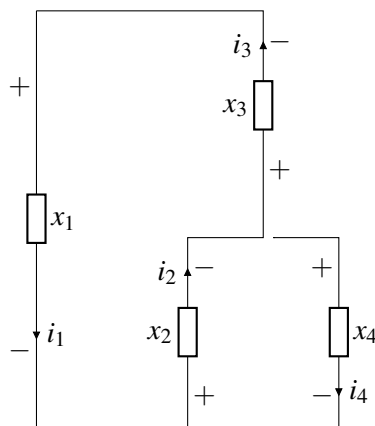

- (a) In the circuit shown above, identify and label all the nodes.
  
- (b) Choose a node to be the reference node and find all the potentials across elements in the circuit in terms of the node potentials you labeled in the previous part
  
- (c) (Optional) Write as many KCL equations as you can for the circuit.

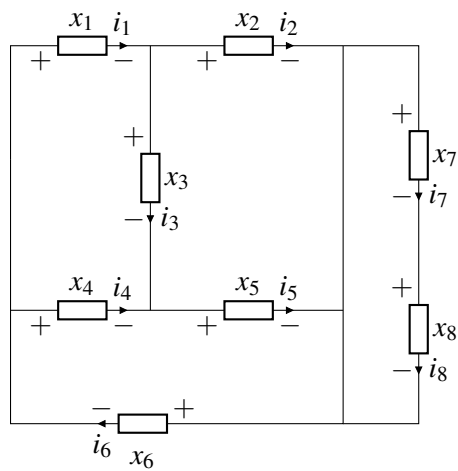(d) (Optional) Write as many KVL equations as you can for the circuit.



(e) In the circuit shown above, identify and label all the nodes.

(f) Choose a node to be the reference node. What is the potential across the elements  $x_6$  and  $x_7$  in terms of node potentials you labeled in the previous part?

(g) (Optional) Write a KCL equation involving  $i_1$  and a KCL equation involving  $i_5$ .

(h) (Optional) Write a KVL equation involving  $V_{x_3}$  and a KVL equation involving  $V_{x_6}$ .