

---


EECS 16A    Designing Information Devices and Systems I

Summer 2023

Discussion 06C


---

### 1. An Inverting Amplifier

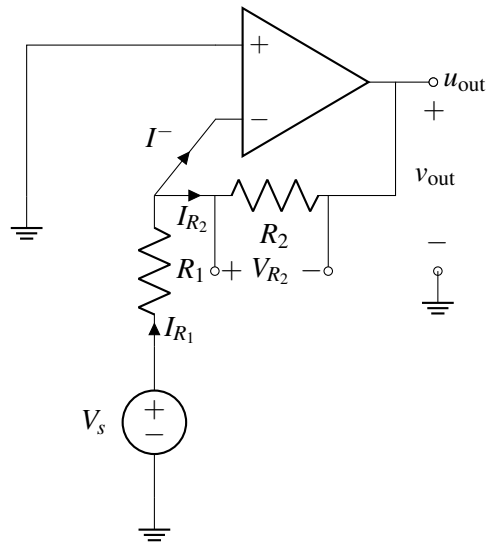

Calculate  $v_{out}$  as a function of  $V_s$  and  $R_1$  and  $R_2$ .

## 2. Multiple Inputs To One Op-Amp

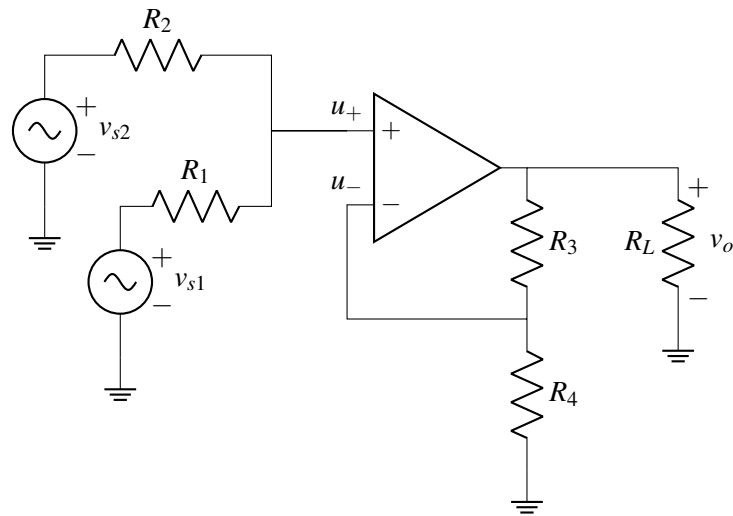

- (a) First, let's focus on the left part of the circuit containing the voltage sources  $v_{s1}$  and  $v_{s2}$ , and resistances  $R_1$  and  $R_2$ . Solve for  $u_+$  in the circuit above. (*Hint: Use superposition.*)

- (b) How would you choose  $R_1$  and  $R_2$  that produce a voltage  $u_+ = \frac{1}{2}V_{s1} + \frac{1}{2}V_{s2}$ ? Could you also achieve  $u_+ = \frac{1}{3}V_{s1} + \frac{2}{3}V_{s2}$ ?

- (c) Now, for the whole circuit, find an expression for  $v_o$ .

- (d) How should we select our values  $R_1, R_2, R_3, R_4$  to find the sum of different signals, i.e.  $V_{s1} + V_{s2}$ ? What about taking the sum and multiplying by 2, i.e.  $2(V_{s1} + V_{s2})$ ?