

Lecture 4C: (7/12/23)



Announcements:

- Module #2 truly begins!
- Office Hours - Mon/Wed 1-2pm in Cory 144MA
Today!
- Lab - Please consider moving from afternoon to evening section
- Today's Topics: How to "solve" a circuit
 - Review of circuit concepts (Note II A)
 - Kirchhoff's Laws (Note II A)
 - Node Voltage Analysis (Note II B)


Node Voltage Analysis

Solve this circuit.
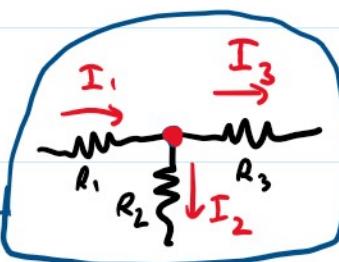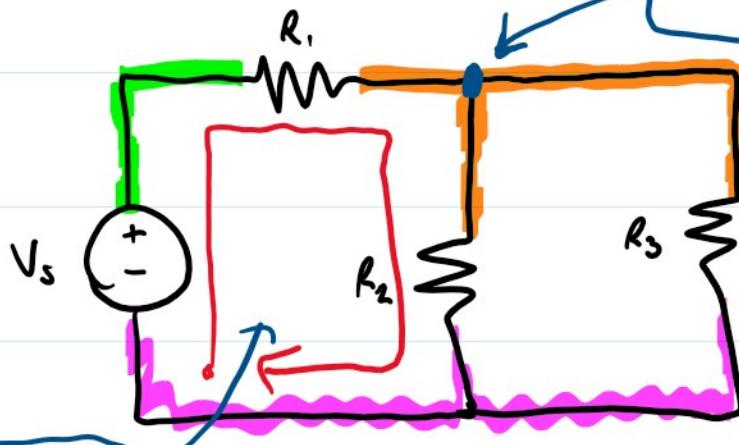
$$\begin{aligned}V_s &= 10V \\R_1 &= 1\Omega \\R_2 &= 2\Omega \\R_3 &= 2\Omega\end{aligned}$$



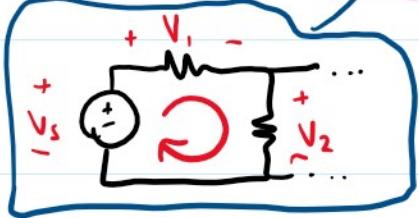What is a node?
How many nodes?
What is V_s ?
What is R ?
Ohm's Law: $V = IR$
How do we "solve"?



What is current?

$$i = \frac{dq}{dt} \leftarrow \text{current is flow of charge}$$

Variable name
i


Unit
A (ampere)

How do we "solve"?

What is charge?

q

C (coulomb)

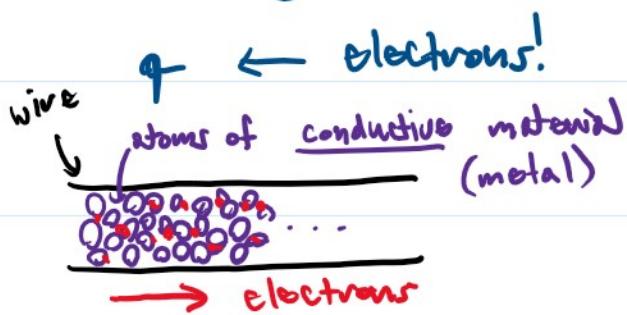

charge of 1 electron is

$$q_e = -1.602 \cdot 10^{-19} C$$

1 coulomb is $6.243 \cdot 10^{18}$ electrons

What is voltage?


V

can make charge move

$$E = q \cdot V$$

↑
energy

potential energy

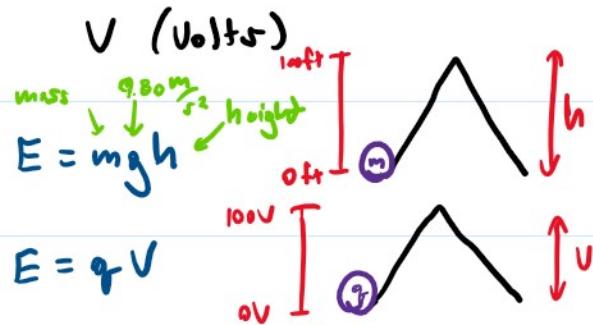

- the amount of energy it takes to move a charge to a new voltage
- Voltage is relative (How high is my hand?)

Node:

A point where two or more circuit elements meet.


A region that is equipotential (equal voltage potential throughout)

Kirchoff's Current Law: "KCL"

1. Sum of currents entering and exiting a node is zero

$$+I_1 - I_2 - I_3 = 0$$

enter exit

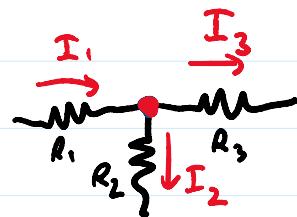

2. Sum of entering currents = sum of exiting currents

$$I_1 = I_2 + I_3$$

enter exit

- Both definitions are equivalent

Loop:


A closed path in a circuit. Ends where it starts.

Kirchoff's Voltage Law: "KVL"

1. Sum of voltages in any loop is zero

$$+V_s - V_1 - V_2 = 0$$

rise drop

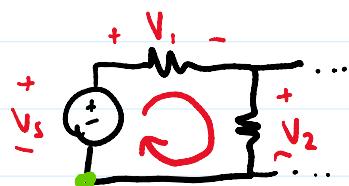

2. Sum of voltage rises = sum of voltage drops

$$V_s = V_1 + V_2$$

rise drop

Elevation
^ — .


$$V_s = V_1 + V_2$$

rise drop

Elevation




Hiking Example:

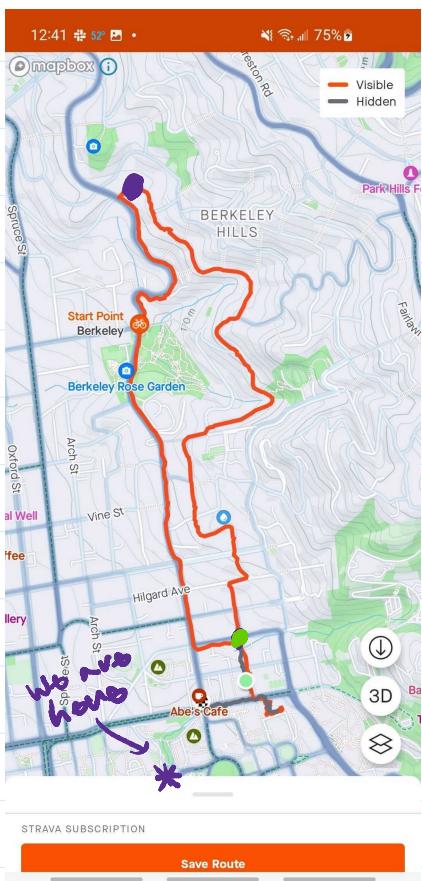

Subscribe for deeper activity analysis features


Elevation

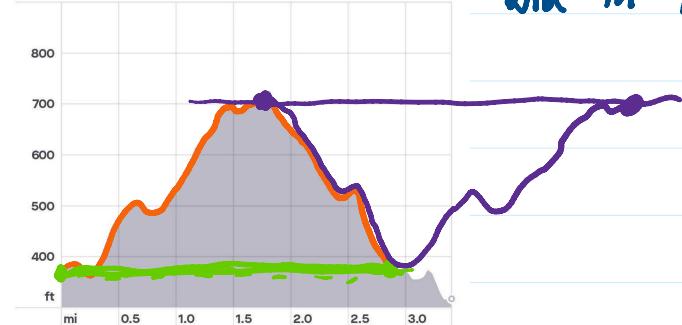

Elevation Gain 457 ft

Max Elevation 732 ft

Pace

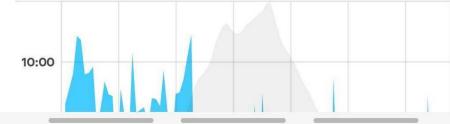


Have to end where I start!
Both in x and y
and in "potential"

Let's solve the circuit using "Node Voltage Analysis"

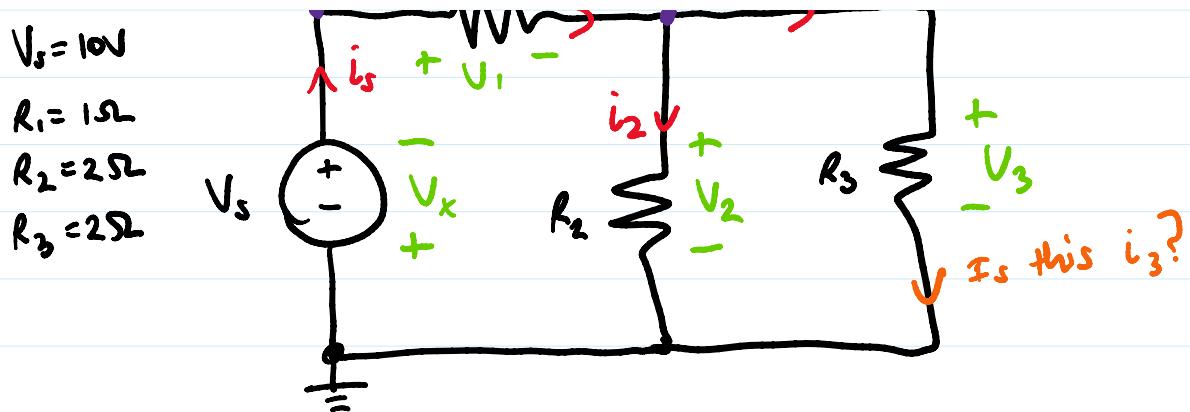"Write a KCL equation at every node in terms of node voltages and IV characteristics." ~ Nathan





Step 1: Pick a reference node ("ground node") \equiv
- can pick ANY node

Step 2: Label all remaining nodes " u_i "
2 nodes $\rightarrow u_1$ and u_2 \leftarrow excludes reference node
remaining

Step 3: Label the current through every element " i_i "


$i_a = i_b$?

KCL: enter = exit
 $i_a = i_b \checkmark$

Step 4: Add voltage labels (+/-) across each element

Passive sign convention:

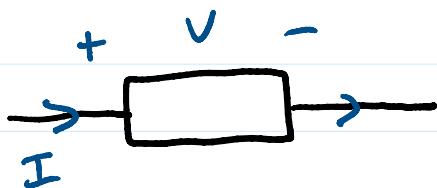current enters positive terminal and exits negative terminal



Step 5: Identify all unknowns. Simplify if possible.

node voltages

$$U_1, U_2$$


these are the important ones

element currents

$$i_x, i_1, i_2, i_3$$

element voltages

$$V_x, V_1, V_2, V_3$$

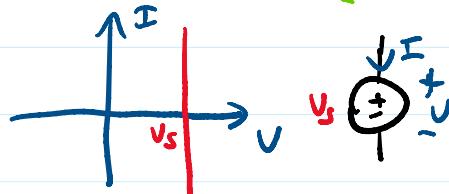

Step 6a: Set up a system of KCL equations

$$\text{At node } U_1: i_5 - i_1 = 0$$

$$\text{At node } U_2: i_1 - i_2 - i_3 = 0$$

Step 6b: Use IV relationships (e.g. Ohm's Law)

$$\left. \begin{array}{l} \text{Element voltages} \\ \text{to} \\ \text{node voltages} \end{array} \right\} \Rightarrow \quad \left\langle \begin{array}{l} \text{I-V characteristics} \end{array} \right.$$

$$V_x = 0 - U_1$$

$$V_1 = U_1 - U_2$$

$$V_2 = U_2 - 0$$

$$V_3 = U_2 - 0$$

$$U_1 = V_s$$

$$U_1 - U_2 = i_1 R_1$$

$$U_2 = i_2 R_2$$

$$U_2 = i_3 R_3$$

$$V_x = -V_5$$

$$V_1 = i_1 R_1$$

$$V_2 = i_2 R_2$$

$$V_3 = i_3 R_3$$

We've eliminated "element voltage" variables!

Step 7: Simplify equations and solve

KCL equations:

$$i_5 - i_1 = 0 \quad ①$$

$$i_1 - i_2 - i_3 = 0 \quad ②$$

I-V equations:

$$\left. \begin{array}{l} U_1 = V_s \\ U_1 - U_2 = i_1 R_1 \\ U_2 = i_2 R_2 \end{array} \right\}$$

$$\boxed{U_1 = V_s} \quad ③$$

$$i_1 = \frac{U_1 - U_2}{R_1}$$

$$i_2 = \frac{U_2}{R_2}$$

$$v_5 - v_1 = v \quad \text{①}$$

$$i_1 - i_2 - i_3 = 0 \quad \text{②}$$

$$\begin{aligned} u_1 - u_2 &= i_1 R_1 \\ u_2 &= i_2 R_2 \\ u_2 &= i_3 R_3 \end{aligned}$$

$$\begin{aligned} i_1 &= \frac{u_1}{R_1} \\ i_2 &= \frac{u_2}{R_2} \\ i_3 &= \frac{u_2}{R_3} \end{aligned}$$

$$\textcircled{1} \quad i_5 - \frac{u_1 - u_2}{R_1} = 0$$

Eliminated element currents!

$$\textcircled{2} \quad \frac{u_1 - u_2}{R_1} - \frac{u_2}{R_2} - \frac{u_2}{R_3} = 0$$

$$\textcircled{3} \quad u_1 = v_5$$

$$V_5 = 10V$$

$$R_1 = 1\Omega$$

$$R_2 = 2\Omega$$

$$R_3 = 2\Omega$$

Matrix vector form: $\vec{A}\vec{x} = \vec{b}$

$$\begin{array}{l} \textcircled{1} \quad \left[\begin{matrix} -\frac{1}{R_1} & \frac{1}{R_1} & 1 \\ \frac{1}{R_1} & -\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right) & 0 \\ 1 & 0 & 0 \end{matrix} \right] \begin{bmatrix} u_1 \\ u_2 \\ i_5 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ V_5 \end{bmatrix} \\ \textcircled{2} \\ \textcircled{3} \end{array}$$

This method ALWAYS works. Let's simplify though.

$$\textcircled{3} \rightarrow \textcircled{2} \quad \frac{V_5 - u_2}{R_1} - \frac{u_2}{R_2} - \frac{u_2}{R_3} = 0$$

$$\frac{V_5}{R_1} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) \cdot u_2$$

$$\boxed{\begin{aligned} V_5 &= 10V \\ R_1 &= 1\Omega \\ R_2 &= 2\Omega \\ R_3 &= 2\Omega \end{aligned}}$$

$$u_2 = \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1} \cdot \frac{1}{R_1} \cdot V_5$$

$$u_2 = \left(\frac{1}{1} + \frac{1}{2} + \frac{1}{2} \right)^{-1} \cdot \frac{1}{1} \cdot 10$$

$$= 1^{-1} \cdot 10$$

$$U_2 = U_1 - U_s$$

$$= 2 \cdot 10$$

$$U_2 = 5V$$


$$U_1 = U_s = 10V$$

③

We've solved the circuit!

check Results:

$$V = iR \rightarrow i = \frac{V}{R}$$

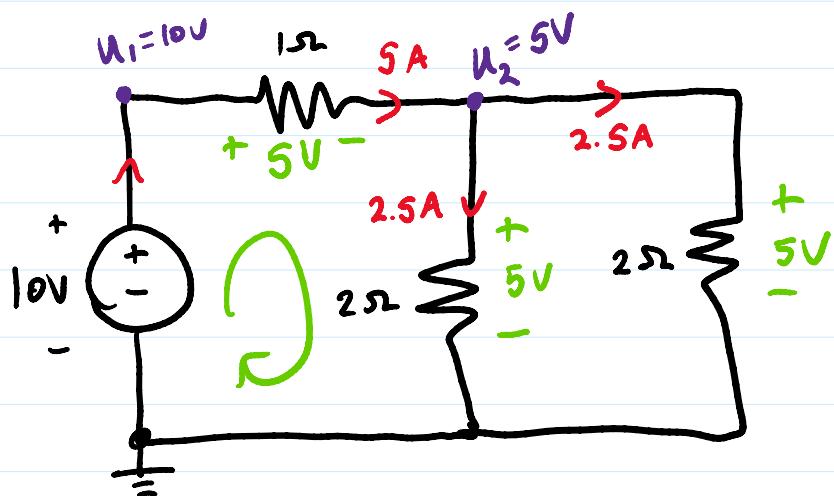

check KCL:

$$@ U_2: 5A = 2.5A + 2.5A \quad \checkmark$$

check KVL

$$+ 10V - 5V - 5V = 0V \quad \checkmark$$