

Lecture 6B: (7/25/23)

Announcements:

- Midterm ← Congrats! !!
 - Midterm Redo due Sunday (7/23) at midnight. (Will be released Wednesday)
 - 2 weeks of lectures left!
 - I will review Midterm on Friday from noon-2pm in Cory 1f4MA
- Final Exam
 - Wednesday (8/9) from 6-9pm in 2040 VLSB
 - Lab Practical on Tuesday (8/8) during normal lab times: 2-5pm and 5-8pm
 - 15% of final exam grade
 - Allotted 30-40 minutes to complete
 - Sign-up for slots will open next week
- Lab - Touch Buttons today
 - For Touch 1 and 2
 - Sign-up on Ed

Today's Topics:


- Comparators (Notes 17)

Very - Topics

- Comparators (Note 17)
- Circuits as Systems
- Dependent Sources (Note 17.3.1)
- Op-amps (Note 17/18)
- Feedback (Note 18)

Operational Amplifier: "op-amp"

5-terminal circuit element

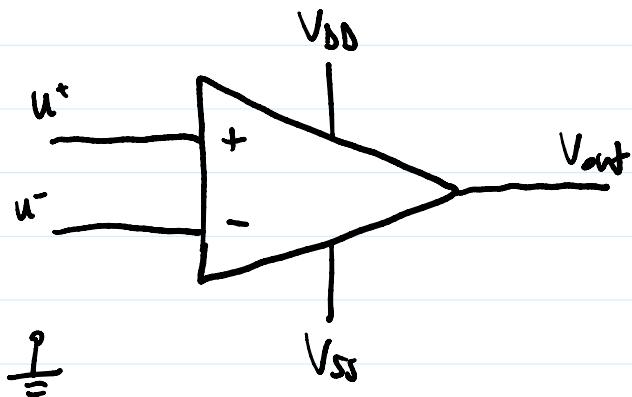

Inputs: u^+ and u^-


Output: V_{out}

Voltage Supply/Rails: $\frac{V_{DD}}{V_{SS}}$

(all are node voltages relative to the reference/zero node)

We will discuss op-amps later
For now we will use as a comparator.


Comparator:

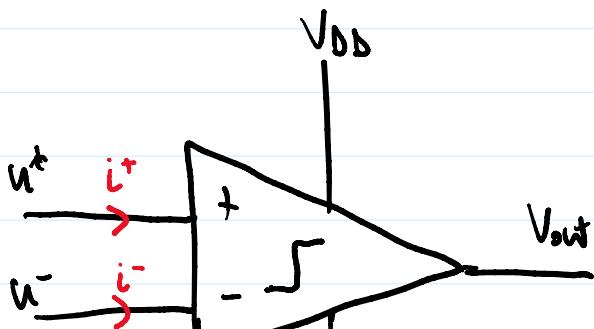

Is input #1 is greater than input #2?

Rules:
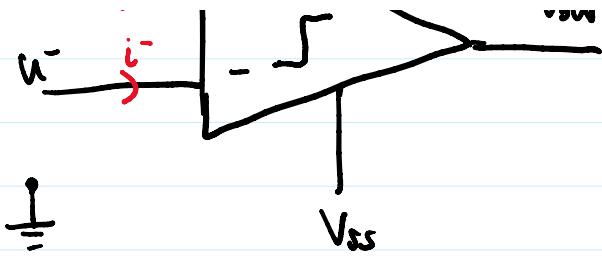
$$1 + L \quad u^+ > u^- \quad \text{then} \quad V_{out} = 1$$




1. If $u^+ > u^-$, then $V_{out} = V_{DD}$
 $(u^+ - u^- > 0)$

2. If $u^+ < u^-$, then $V_{out} = V_{SS}$
 $(u^+ - u^- < 0)$

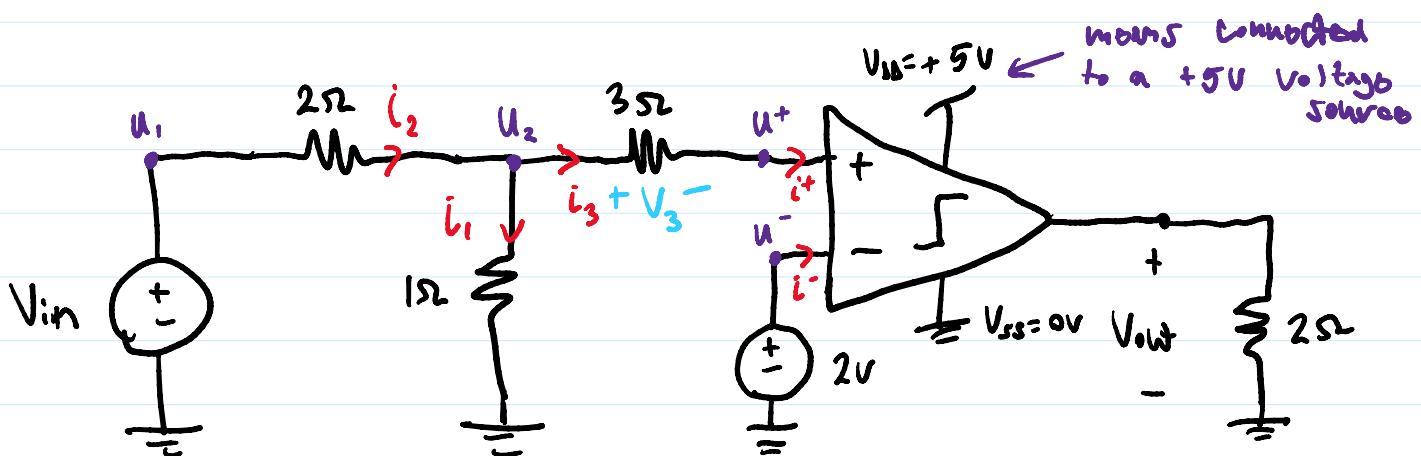3. $i^+ = i^- = 0$ ALWAYS

Ex). Find V_{out} as a function of V_{in}



$$i^+ = i^- = 0 \rightarrow i_3 = 0 \rightarrow V_3 = 0 \rightarrow u_2 = u^+$$

$u_1 = V_{in}$

NVA: KCL at node u_2 : $i_2 - i_1 - i_3 = 0$

$$\frac{u_1 - u_2}{2\Omega} - \frac{u_2 - 0}{1\Omega} - 0 = 0 \rightarrow \frac{1}{2}V_{in} - \frac{3}{2}u_2 = 0 \rightarrow u_2 = \frac{1}{3}V_{in}$$

For a comparator we need to focus on when
 $u^+ > u^-$ and $u^+ < u^- \rightarrow u^+ = u^-$

If $u^+ > u^- \rightarrow V_{out} = V_{DD} = +5V$


$$u^+ = \frac{1}{3}V_{in} \rightarrow V_{in} = 6V$$

If $u^+ > u^- \rightarrow V_{out} = V_{DD} = +5V$


If $u^+ < u^- \rightarrow V_{out} = V_{SS} = 0V$

$$u^+ = \frac{1}{3} V_{in} \rightarrow V_{in} = 6V$$
$$u^- = 2V \rightarrow$$

↑
transition point

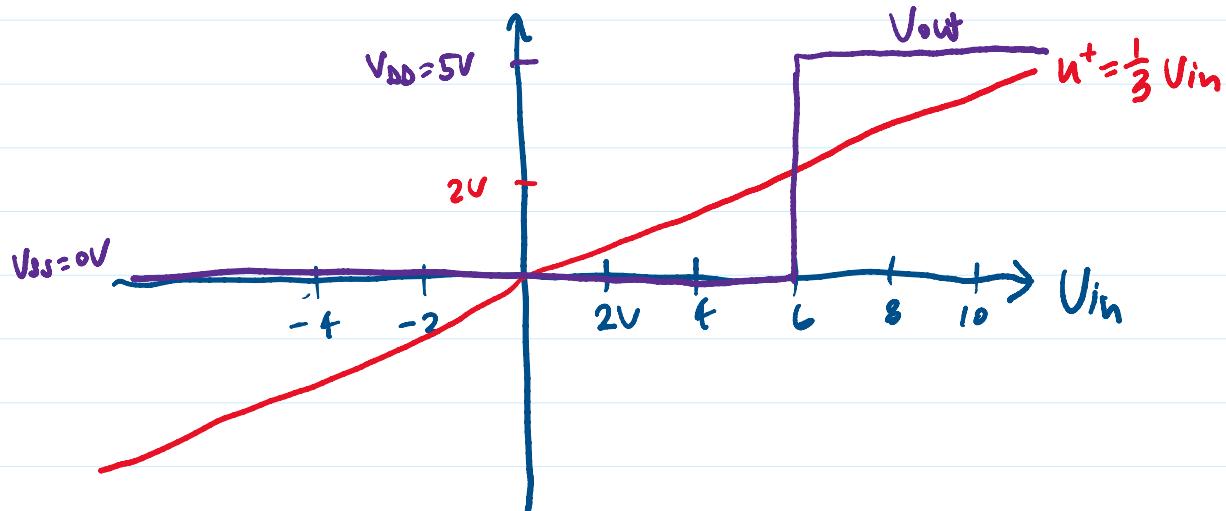

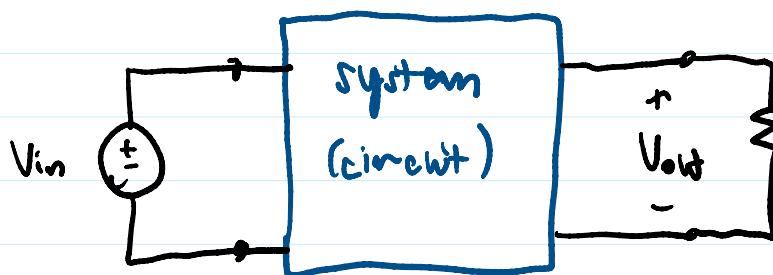Circuit as a system: (with input and output)



Block Diagram



A is scalar
↓

$$V_{out} = A \cdot V_{in}$$

output = gain · input

Ex). Gain of system $\rightarrow A = \frac{1}{4}$

What if we want $V_{out} = 2V$?

~~then $V_{in} = 4V$~~

LINEAR

What about $V_{out} = 1V$?

$V_{in} = 4V$

What if we want $V_{out} = 2V$?

- We would choose $V_{in} = 8V$

What about $V_{out} = 1V$?


$V_{in} = 4V$

Can we design a circuit with a gain of $A = \frac{1}{4}$?

Ex). Voltage Divider

$$V_{out} = \frac{R_2}{R_1 + R_2} \cdot V_{in} = \frac{1}{4} V_{in}$$


$\underbrace{\qquad\qquad\qquad}_{A}$

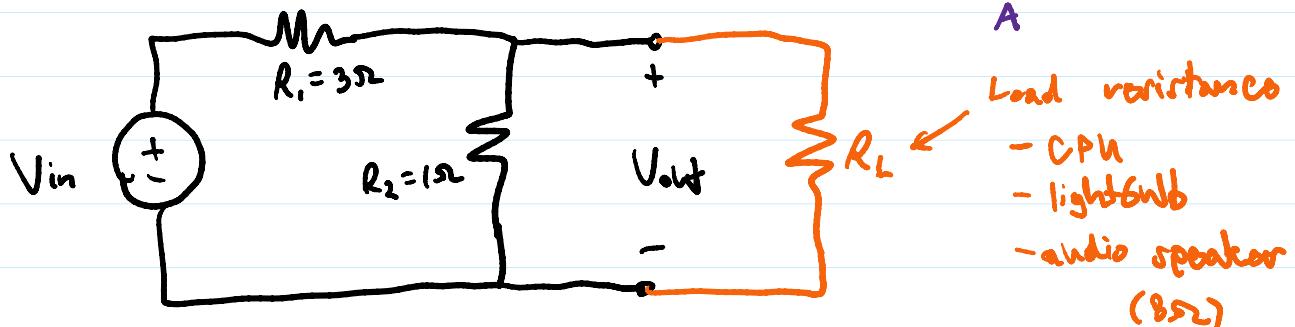

What's the problem? Adding a load (or more load) makes V_{out} drop

We need a circuit where $A = \frac{V_{out}}{V_{in}}$ does not depend on the amount of loading.

Dependent Sources: (Notes 17.3.1)

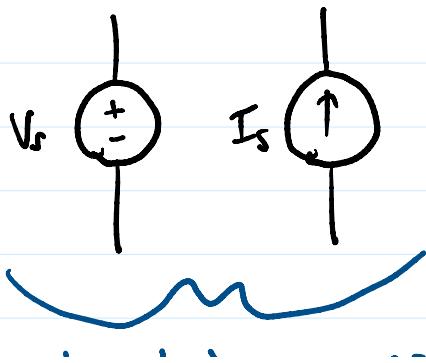


scaling of a
Voltage (or current)
in the circuit

$$\alpha \cdot V_x$$

OR

$$\beta \cdot I_x$$

Dependent

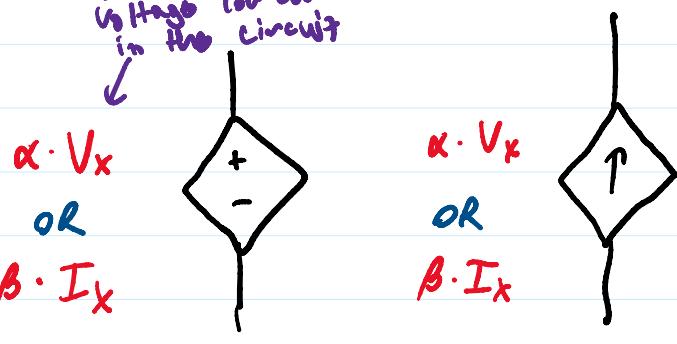

Independent sources


V_s and I_s are independent of the rest of the circuit

Dependent voltage source

Dependent on the rest of the circuit

Dependent current source

Ex). Find V_k

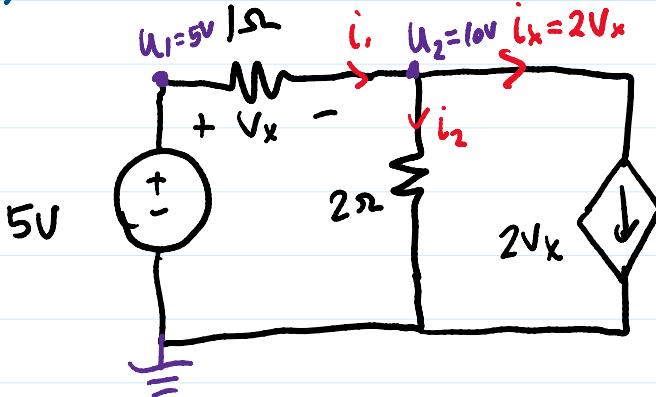

$$\text{KCL at } U_2: i_1 - i_2 - i_x = 0$$

$$① \frac{U_1 - U_2}{1\Omega} - \frac{U_2 - 0}{2\Omega} - 2V_x = 0$$

$$U_1 = 5V \quad ②$$

$$V_x = U_1 - U_2 \quad ③$$

$$V_x = 5V - 10V$$

$$V_k = -5V$$



Substitute ② and ③ into ①

$$\frac{5 - U_2}{1} - \frac{U_2}{2} - 2 \cdot (5 - U_2) = 0 \rightarrow 5 - 10 = (1 + \frac{1}{2} - 2) \cdot U_2$$

$$U_2 = \frac{-5}{-0.5} = 10V$$

Return to our earlier system:

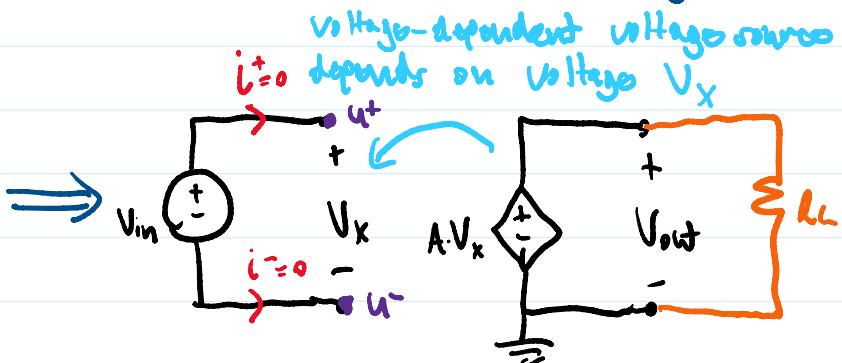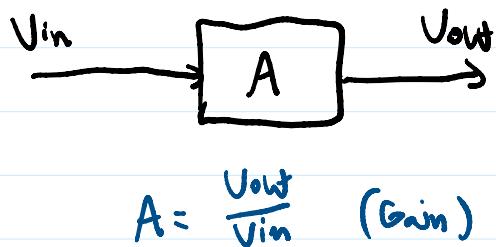How could we implement this with a dependent voltage source?




Does R_L affect V_{out} ? No!

$$V_{out} = A \cdot V_x = A \cdot (u^+ - u^-)$$

$$= A \cdot V_{in} \quad \checkmark$$

Operational Amplifier: "op-amp"

Internal op-amp model:

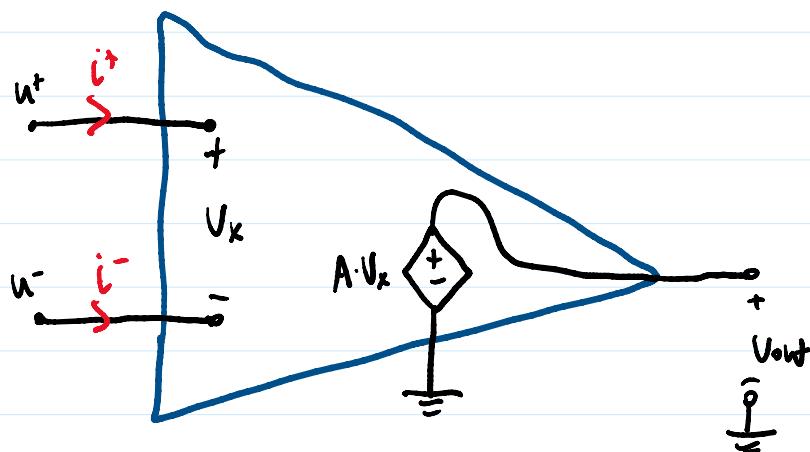

V_x is difference of inputs
↓

$$V_{out} = A \cdot V_x = A \cdot (u^+ - u^-)$$

Golden Rule #1:
 $i^+ = i^- = 0$

It doesn't matter what is connected to u^+ and u^- externally.
 i^+ and i^- are ALWAYS zero.

We did it! Unfortunately, no "

All op-amps have internal values of gain "A" which are:

1) very large $\rightarrow A > 1000 \rightarrow A > 1 \cdot 10^6$


2) no insprecision \rightarrow Two op-amps in the batch could have " $A = 1 \cdot 10^6$ " and " $A = 1.1 \cdot 10^6$ "

How do we achieve the V_{out} we want when we can't know the exact value of the gain "A"?

Feedback:

Use information about the output of a system to "feed" back into the input of a system.

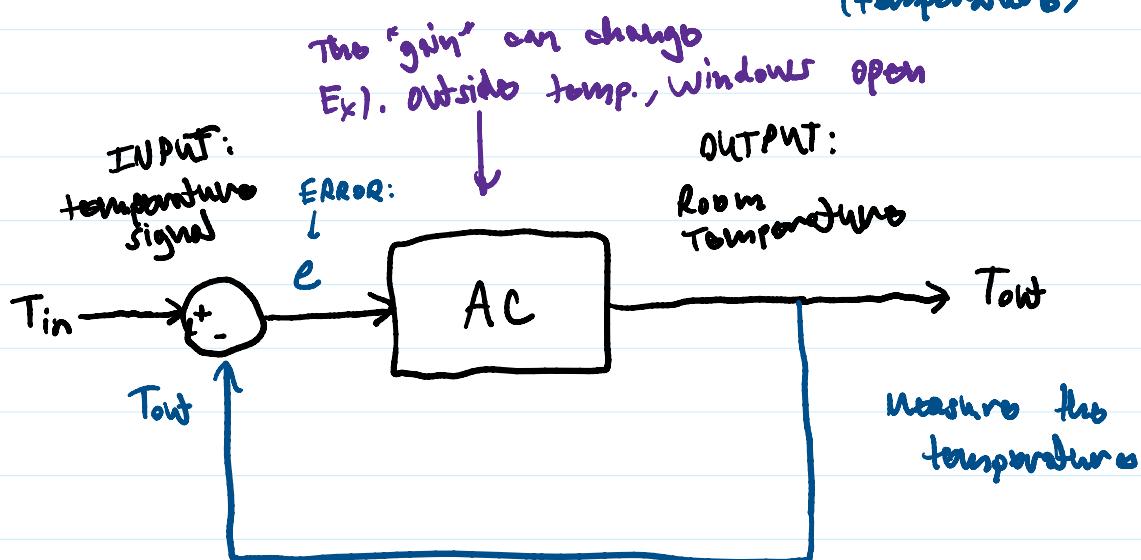
Ex). Thermostat \leftarrow control the air conditioning (AC) (temperature)



Feedback lets temperatures to correct it too hot or too cold

What's the math behind feedback? \rightarrow Control Theory
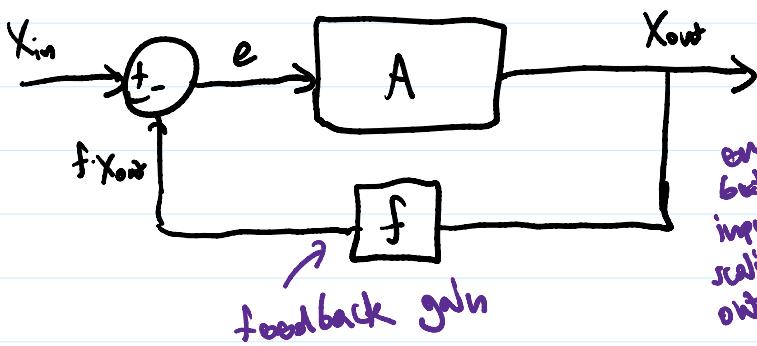
$$\text{Before: } \frac{x_{out}}{x_{in}} = A$$



After feedback:

$$e = x_{in} - f x_{out}$$

error between input and output \rightarrow substitute $x_{out} = A \cdot e$

$$x_{out} = A \cdot (x_{in} - f x_{out})$$

| move x_{out} to

feedback J...

out

$$X_{out} = A \cdot (X_{in} - f X_{out})$$

↓ Move X_{out} to
one side

What if A is very large? ($A \gg 1$)

Ex). $A = 1000$

$$\frac{X_{out}}{X_{in}} = \frac{1000}{1 + 1000f} \approx \frac{1000}{1000f} = \frac{1}{f}$$

As $A \rightarrow \infty$

$$\lim_{A \rightarrow \infty} \frac{X_{out}}{X_{in}} = \lim_{A \rightarrow \infty} \frac{A}{1+Af} = \lim_{A \rightarrow \infty} \frac{A}{Af}$$

$$\lim_{A \rightarrow \infty} \frac{X_{out}}{X_{in}} = \frac{1}{f}$$

$$(1 + Af) \cdot X_{out} = A \cdot X_{in}$$

$$\frac{X_{out}}{X_{in}} = \frac{A}{1 + Af}$$

Black's
Formula

{ We changed the system gain from
"A" to " $\frac{A}{1+Af}$ ". So what?

This is the essence of feedback. "A" is unknown, but we can control the input "X_{in}" and feedback gain "f" to control the overall gain and ultimately set the desired output "X_{out}".

How do we implement feedback gain "f"? Using circuits