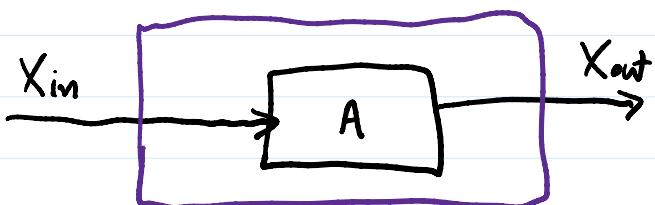


Lecture 6C: (7/26/23)Announcements:


- Discussion - Cheating Attendance

Today's Topics:

- Feedback
- Solving Op-amp circuits } (Note 18)
- Non-inverting op-amp circuit } (Note 19)
- Negative Feedback Test } (Note 18/19)
- Using an op-amp circuit (Note 18/19)
- Inverting op-amp circuit (Note 18.b)

Feedback (cont.)
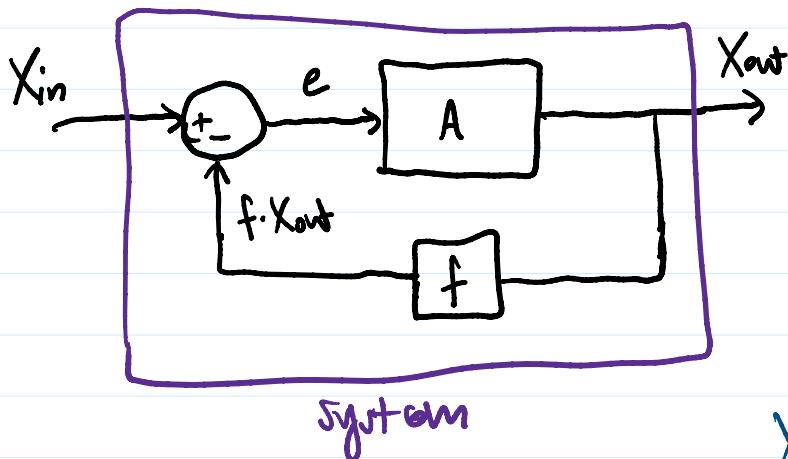
$$\text{Before: } \frac{X_{out}}{X_{in}} = A$$



After (feedback):

$$\frac{X_{out}}{X_{in}} = ?$$

$$e = X_{in} - f \cdot X_{out} \quad ) \text{ substitute}$$

$$X_{out} = A \cdot e$$

$$X_{out} = A \cdot (X_{in} - f \cdot X_{out})$$

System

$$X_{out} = A \cdot (X_{in} - f \cdot X_{out})$$

What if  $A$  is very large? ( $A \gg 1$ )

Ex).  $A = 1000$

$$\frac{X_{out}}{X_{in}} = \frac{1000}{1 + 1000f} \approx \frac{1000}{1000f} = \frac{1}{f}$$

As  $A \rightarrow \infty$

$$(1 + Af) \cdot X_{out} = A \cdot X_{in}$$

$$\frac{X_{out}}{X_{in}} = \frac{A}{1 + A \cdot f}$$

Block's  
Formula

We changed the system gain from " $A$ " to " $\frac{A}{1 + Af}$ ". So what?

$$\lim_{A \rightarrow \infty} \frac{X_{out}}{X_{in}} = \lim_{A \rightarrow \infty} \frac{A}{1 + Af} = \lim_{A \rightarrow \infty} \frac{A}{Af}$$

$$\lim_{A \rightarrow \infty} \frac{X_{out}}{X_{in}} = \frac{1}{f}$$


This is the essence of feedback. " $f$ " is unknown, but we can control the input " $X_{in}$ " and the feedback gain " $f$ " to control the overall gain and set the desired " $X_{out}$ ".

How do we implement " $f$ "? Using circuit

Let's apply feedback to our op-amp:

Can we make  $\frac{V_{out}}{V_{in}} = 1$ ?

Connect  $V_{out}$  to  $u^-$  terminal

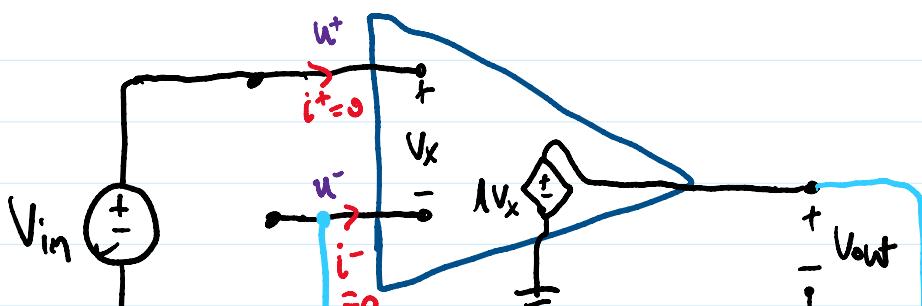

Solve the circuit:

$$u^+ = V_{in} \quad u^- = V_{out}$$

$$V_{out} = A \cdot V_x = A \cdot (u^+ - u^-)$$

$$V_{out} = A \cdot (V_{in} - V_{out})$$

$V_{in}$



$\frac{+}{-} V_{out}$

$$V_{out} = A \cdot (V_{in} - V_{out})$$

$$(1+A) \cdot V_{out} = A \cdot V_{in}$$

$$V_{out} = \frac{A}{1+A} V_{in}$$

$\downarrow A \rightarrow \infty$

$$\boxed{V_{out} = V_{in}}$$

We know op-amps have a large value of "inferred gain" "A"


What does this result mean?

$$u^+ = V_{in} \quad u^- = V_{out} \approx V_{in} \rightarrow \text{Thus, } u^+ \approx u^-$$

Golden Rule #2:

If the op-amp circuit is in negative feedback,  
then  $u^+ = u^-$

What is the point of this circuit?

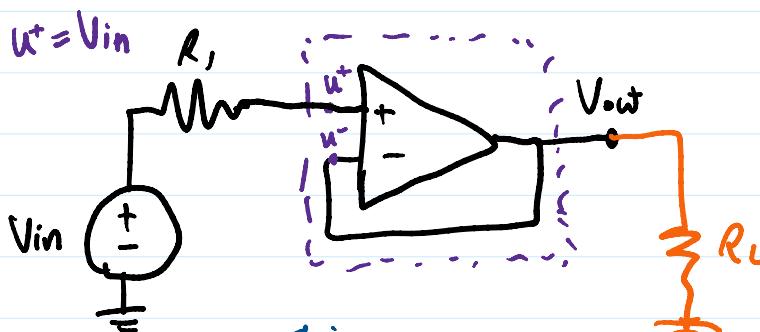


This op-amp configuration is called a unity-gain buffer



$V_{out}$  will **ALWAYS** be  $= V_{in}$  no matter the value of resistance  $R_L$

This circuit decouples  $V_{out}$  from  $V_{in}$ .

$$P_{R_L} = \frac{V_{out}^2}{R_L}$$

Non-inverting op-amp circuit:

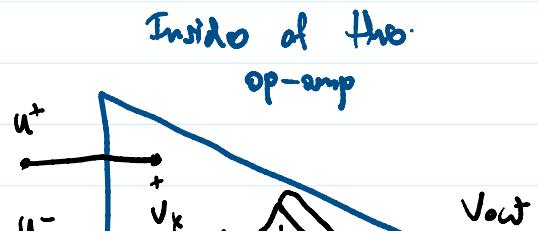

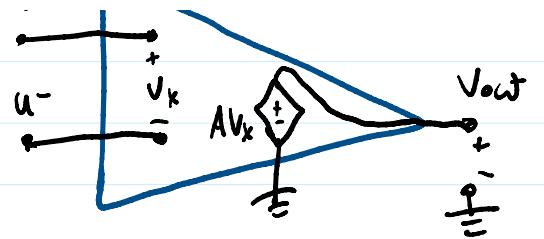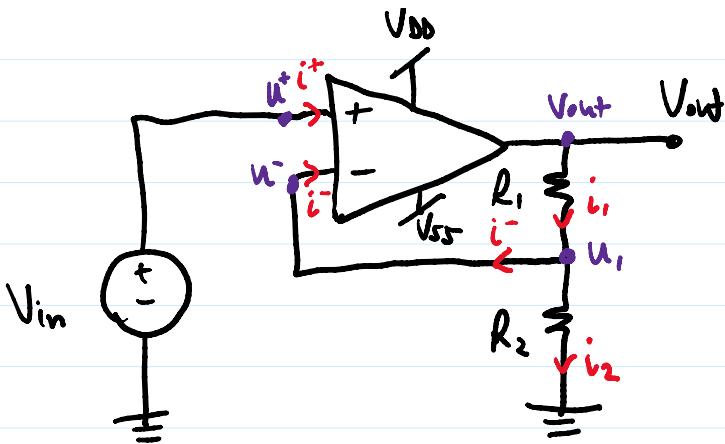

$$V_{\text{out}} = A \cdot V_x = A \cdot (u^+ - u^-)$$

↑  
 large gain  
 ↑  
 difference of inputs

Method #1:

The complete way using only Golden Rule #1:  $i^+ = i^- = 0$

Using NVA: Label unknown nodes:  $u^+, u^-, u_+, V_{\text{out}}$   
 $= V_{\text{in}}$        $\uparrow$   
 $u^- = u_+$

KCL @ node  $u_+ = u^-$ :

$$i_+ - i^- - i_2 = 0$$

$$\frac{V_{\text{out}} - u_1}{R_1} - i^- - \frac{u_1 - 0}{R_2} = 0$$

From GR #1:  $i^- = 0$

$$\frac{V_{\text{out}}}{R_1} = \left( \frac{1}{R_1} + \frac{1}{R_2} \right) u_1$$

$$u_1 = u^-$$

$$V_{\text{out}} = \left( 1 + \frac{R_1}{R_2} \right) u^-$$

$$V_{\text{out}} = A \cdot (u^+ - u^-) \rightarrow u^- = u^+ - \frac{1}{A} V_{\text{out}}$$

$$u^+ = V_{\text{in}} \longrightarrow = V_{\text{in}} - \frac{1}{A} V_{\text{out}}$$

$$V_{\text{out}} = \left( 1 + \frac{R_1}{R_2} \right) \cdot \left( V_{\text{in}} - \frac{1}{A} V_{\text{out}} \right)$$

$$A \rightarrow \infty$$

$$V_{\text{out}} = \left( 1 + \frac{R_1}{R_2} \right) \cdot V_{\text{in}}$$

Gain of the non-inverting op-amp:  $\frac{V_{\text{out}}}{V_{\text{in}}} = \left( 1 + \frac{R_1}{R_2} \right) = G$

$G \geq 1 \leftarrow$  can "boost" input voltage

$G \geq 1 \leftarrow$  can "boost" input voltage

Pick  $R_1 = 2\Omega$ ,  $R_2 = 1\Omega$

$$V_{out} = \left(1 + \frac{2\Omega}{1\Omega}\right) \cdot V_{in}$$

$$= 3 \cdot V_{in}$$


Pick  $R_1 = 10\Omega$ ,  $R_2 = 5\Omega$

$$V_{out} = \left(1 + \frac{10\Omega}{5\Omega}\right) \cdot V_{in}$$

$$= 3 \cdot V_{in}$$

An op-amp cannot output a  $V_{out} > V_{DD}$  or  $V_{out} < V_{SS}$ . Beyond these limits, the output saturates.
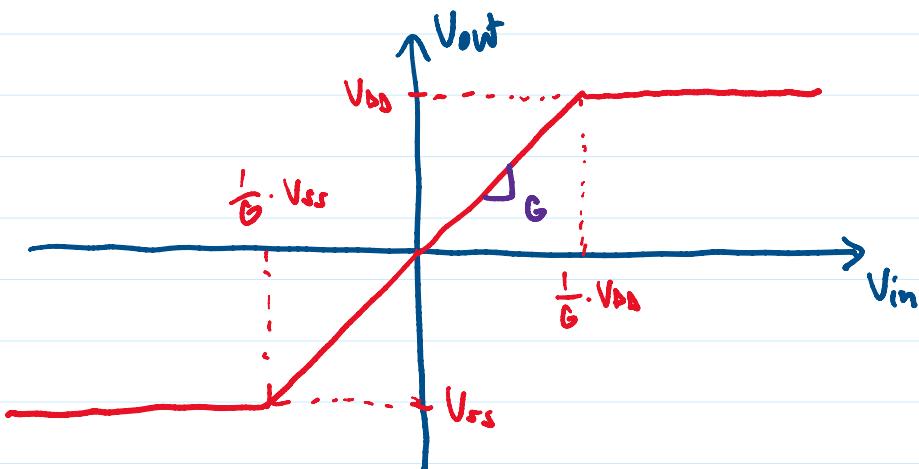
$$V_{out} = \begin{cases} V_{DD} & \text{if } V_{out} > V_{DD} \\ G \cdot V_{in} & \text{if } V_{SS} < V_{out} < V_{DD} \\ V_{SS} & \text{if } V_{out} < V_{SS} \end{cases}$$



Method #2:

The faster way using both Golden Rules #1 and #2

- Requires test for negative feedback  $i^+ = i^- = 0$        $u^+ = u^-$

Using NVA: Label unknown nodes:  $u^+, u^-, u_i, V_{out}$

KCL @ node  $u_i = u^-$ :

$$i_1 - i^- - i_2 = 0$$

$$V_{in} = \underbrace{u^+}_{\text{GR #2}} = \underbrace{u^-}_{\text{GR #2}} = u_i$$

$$v_1 - v_2 = 0$$

GR #2

$$\frac{V_{out} - u_1}{R_1} - 0 - \frac{u_1 - 0}{R_2} = 0 \quad GR \#1: i = 0$$

$$V_{out} = \left(1 + \frac{R_1}{R_2}\right) u_1$$

$$V_{out} = \left(1 + \frac{R_1}{R_2}\right) \cdot V_{in}$$

$$u_1 = u^- = u^+ = V_{in}$$

How do we determine if a circuit is in negative feedback?

### Negative Feedback Test

We can test any circuit for negative feedback by using a "perturb and observe" or "wiggle" or "dink" method


Step 1: Null independent sources

Voltage sources  $\rightarrow$  short circuits


Current sources  $\rightarrow$  open circuits

Step 2: Perturb the output and observe how it propagates through the loop back to the output

Ex). Unity gain buffer

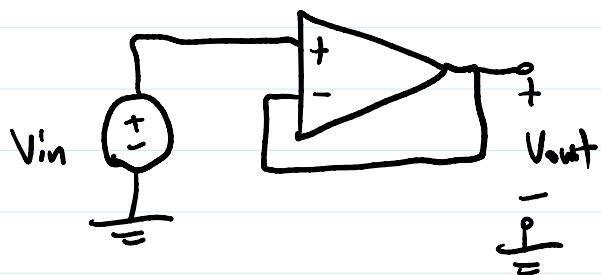


Step 1  
⇒

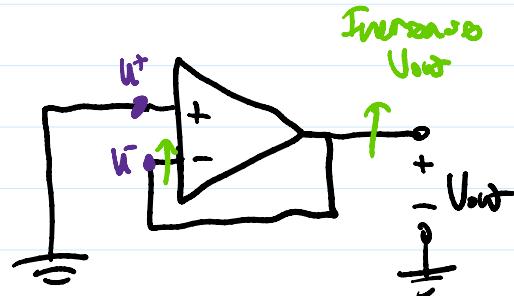

Remember that  $V_{out} = A(u^+ - u^-)$

$=$  $\frac{1}{A}$  $=$  $\frac{1}{A}$ 


Remember that  $V_{out} = A(u^+ - u^-)$

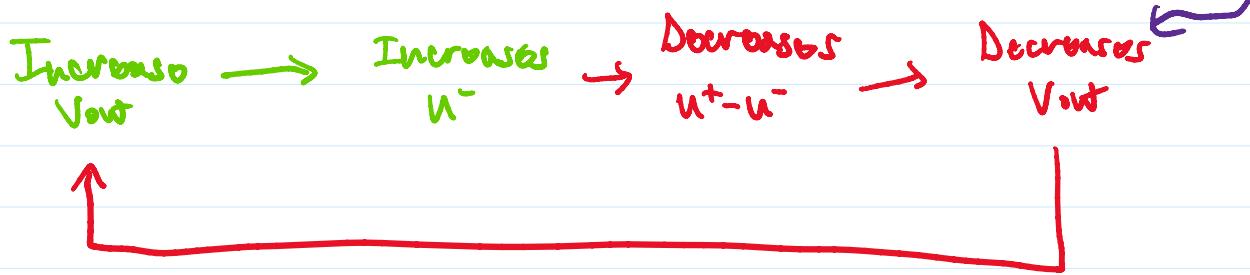

An increase in  $V_{out}$  causes a decrease in  $V_{out}$   
 $\rightarrow$  self-correcting  $\leftarrow$  negative feedback

Back to the non-inverting op-amp:

Negative Feedback Test:

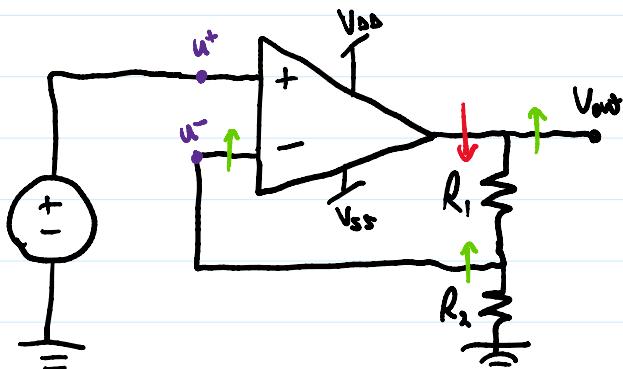

Passes negative  
feedback test

