

## Lecture 6D (7/26/23):

### Announcements:


- Last day of Module #2 ↪
- Module #3 next week ← Learn how GPS works
- Midterm Review tomorrow from noon-2pm in Cory 144MA
- Midterm Redo due Sunday night
- Lab - Touch 3 tonight ← Long lab!

### Today's Topics:

- Inverting op-amp circuit (Notes 18.6)
- Circuit Design (Notes 20)
- Using an op-amp circuit (Notes 18/19)
- Capacitor Touch circuit (Notes 20)

### Inverting op-amp circuit:


Find  $\frac{V_{out}}{V_{in}} = G$

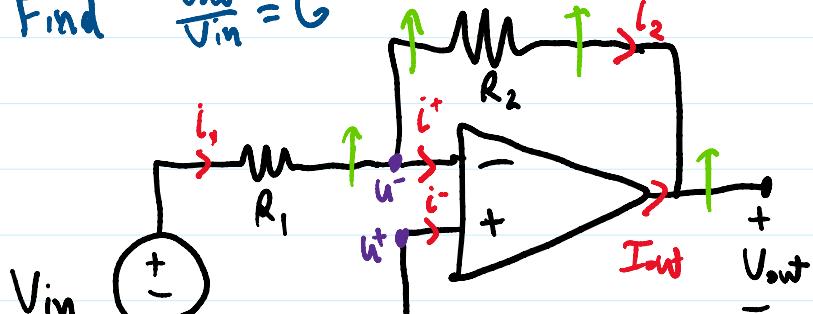

Negative feedback test:

Increase  $V_{out}$   
↓

Increase  $u_-$   
↓

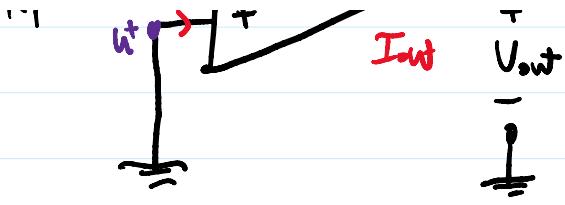

$$V_{out} = A \cdot (u^+ - u^-)$$

increases  $u^+$



Decrease  $u^- - u^+$



Decrease  $V_{out}$

Answers to fit (NF) ✓

KCL @  $u^-$ :

$$i_1 - i^- - i_2 = 0$$

$$GR \#1: i^- = 0$$

$$\frac{V_{in} - u^-}{R_1} - 0 - \frac{u^- - V_{out}}{R_2} = 0 \quad GR \#2: u^- = u^+ \text{ since NF}$$

$$u^+ = 0$$

$$\frac{V_{in}}{R_1} + \frac{V_{out}}{R_2} = 0$$

$$V_{out} = -\frac{R_2}{R_1} V_{in}$$

$$\text{Gain of inverting op-amp: } \frac{V_{out}}{V_{in}} = -\frac{R_2}{R_1} = G$$

can negative (current)  $\rightarrow G \leq 0$


the input voltage

Aside: When applying NVA to op-amp circuits, do NOT write a KCL equation at the output. This is because we do not know  $I_{out}$  (it depends on the rest of the circuit).

Circuit Design: ← Ambiguous like proofs in Module #1  
(Note 20)

Step 1: Specify Design Goals

Step 2: Describe a Strategy

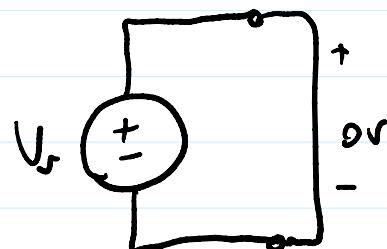


Step 2: Describe a strategy




Step 3: Implement Strategy

$$V = IR = \infty \cdot 0$$

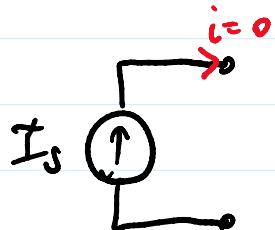Step 4: Verify whether solution is consistent



Using an op-amp circuit:

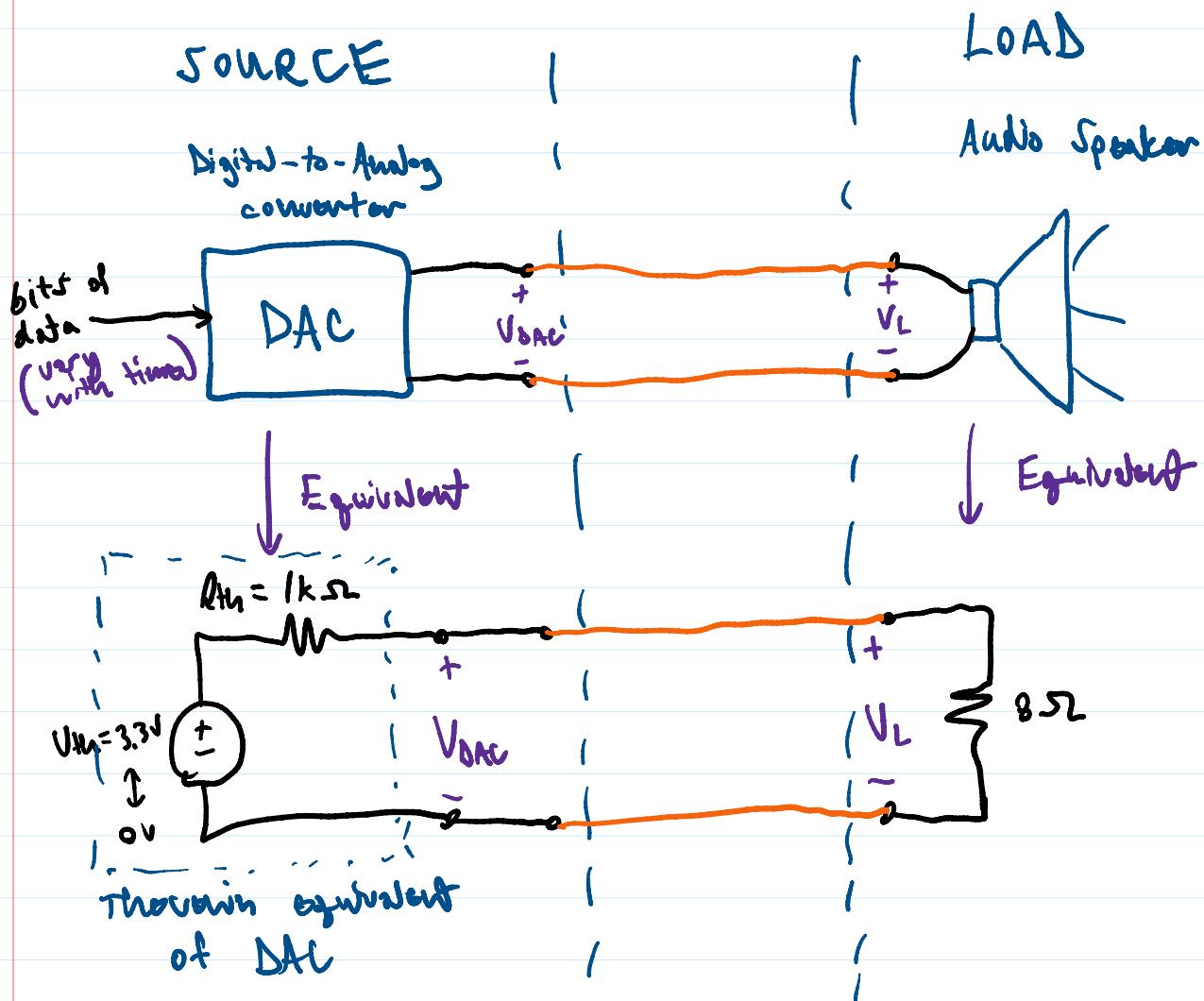


Design Step 1: Let's try to turn our bits of audio data

Design Step 1: Let's try to turn our bits of audio data into audible music.

First, let's connect the DAC directly to the speaker.

$$\rightarrow V_L = V_{DAC}$$

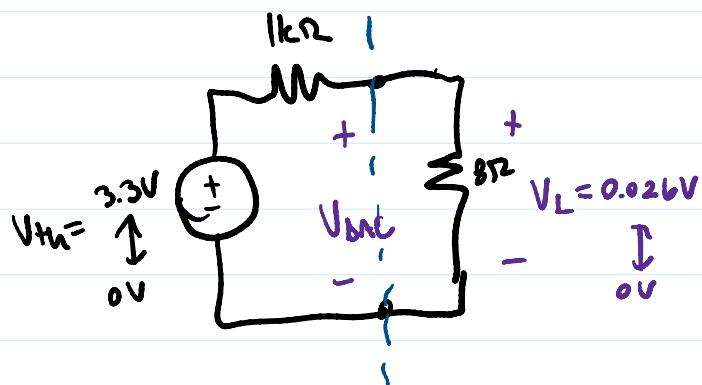


$$V_L = \frac{8\Omega}{1k\Omega + 8\Omega} \cdot V_{HH}$$

$$= 0.0079 \cdot (3.3V) = 0.026V$$

We need this voltage to be 10V to drive the speaker


Design Step 2:

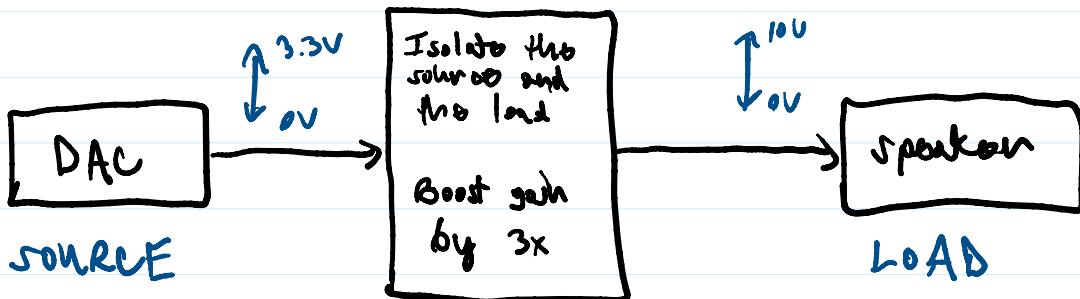


Let's use a  
non-inverting op-amp!

Design Step 3: Implement

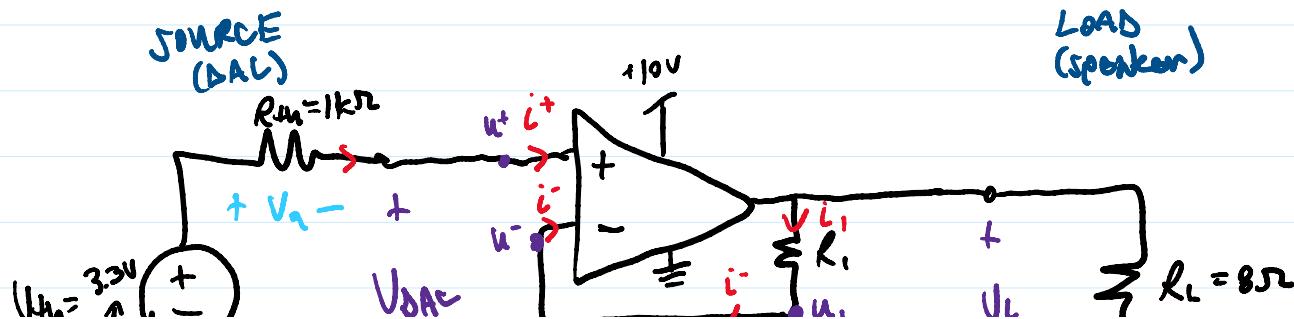We need to map:  $V_{DAC} = 0V \rightarrow 3.3V \rightarrow V_L = 0V \rightarrow 10V$



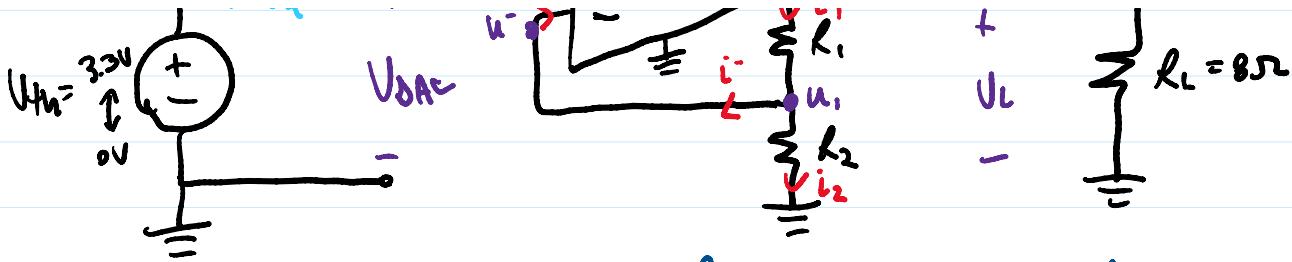


$$V_{out} = \left(1 + \frac{R_1}{R_2}\right) \cdot U_{in}$$

$$= 3 \cdot U_{in}$$

Pick  $R_1 = 2k\Omega$   
 $R_2 = 1k\Omega$

Design Step 4: Check Consistency
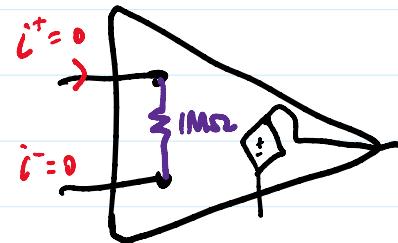
$$GR \#1: i^+ = 0 \rightarrow U_n = 0 \rightarrow U^+ = U_{DAC} = U_{DH} = 3.3V$$



Negative Feedback:  $GR \#2: U^- \approx U^+ = U_{DH} \rightarrow U_1 = U^- = U_{DH}$

$$KCL @ u_1: i_1 - i^- - i_2 = 0 \quad \leftarrow GR \#1: i^- = 0$$

$$\frac{U_L - U_1}{R_1} - 0 - \frac{U_1 - 0}{R_2} = 0 \rightarrow U_L = R_1 \cdot \left(\frac{1}{R_1} + \frac{1}{R_2}\right) \cdot U_1$$


$$U_L = \left(1 + \frac{R_1}{R_2}\right) \cdot 3.3V$$

$$10V = G \cdot 3.3V$$

$$= \underbrace{\left(1 + \frac{2k\Omega}{1k\Omega}\right)}_3 \cdot 3.3V \approx 10V \checkmark$$

### Designing a circuit for capacitive touch:

Recall from capacitive touch:

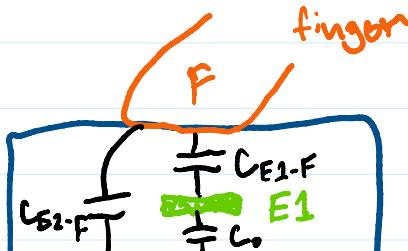

Equivalent capacitance  
between nodes  $E_1$  and  $E_2$

Before touch:  $C_E = C_0$

After touch:  $C_E = C_0 + (C_{E1-F} \parallel C_{E2-F})$




$$\begin{aligned} \text{After touch: } C_e &= C_0 + (C_{E1-F} \parallel C_{E2-F}) \\ &= C_0 + C_\Delta \end{aligned}$$

The equivalent capacitance increases when there is a touch


Design Step #1 { How do we measure a change in capacitance?

Design Step #2:

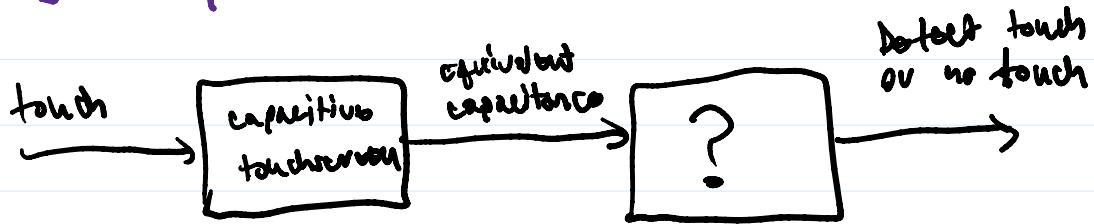



Design Step #3:

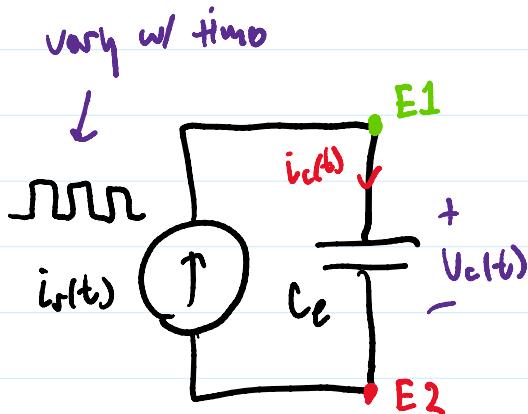Convert the equivalent capacitance to a current source



$$i_c(t) = C_e \frac{dV_c(t)}{dt} \rightarrow V_c(t) = \int i_c(t) dt$$

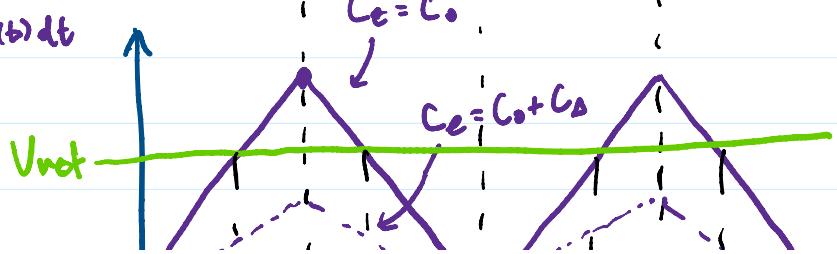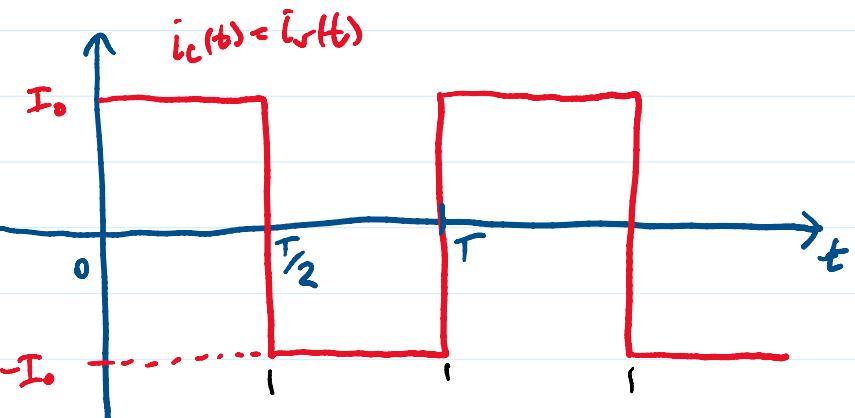①  $i_c(t) = I_0 > 0$   
so capacitor is charging



$$(1) i_c(t) = I_0 > 0$$

so capacitor is charging

$$V_{c(t)} = + \frac{1}{C_e} I_0 \cdot (t - t_0) + V_{c(t_0)}$$

Increasing linearly with time





$$(2) i_c(t) = -I_0 < 0$$

so capacitor is discharging

$$V_{c(t)} = - \frac{1}{C_e} I_0 \cdot (t - t_0) + V_{c(t_0)}$$

Decreasing linearly with time

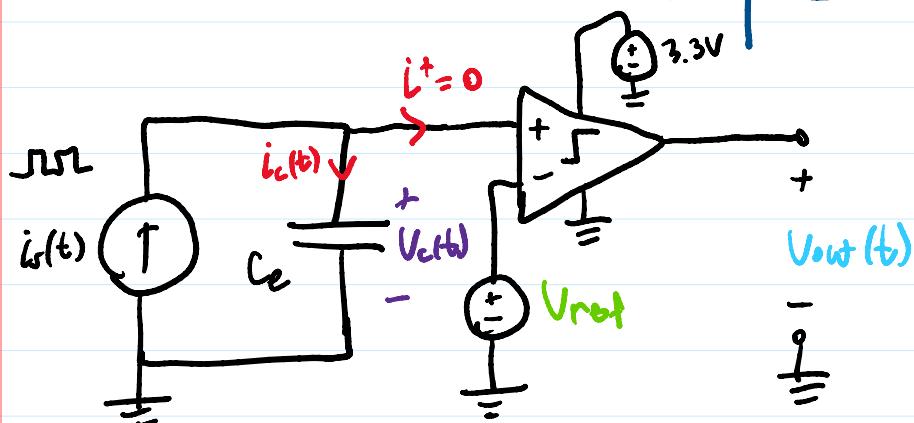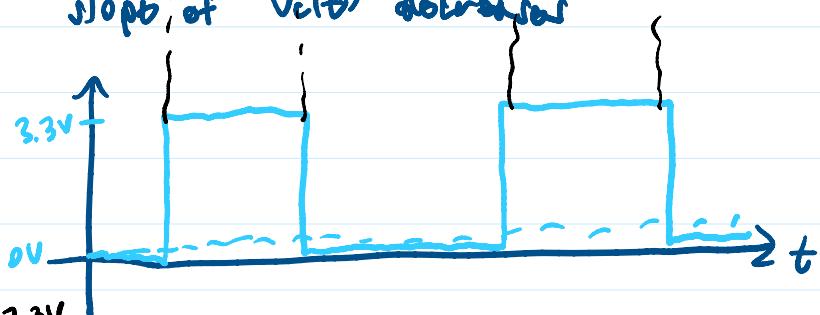
If touch, then  $C_e$  increases and slope of  $V_{c(t)}$  decreases



If touch, then the comparator output is zero.  
If no touch, then  $V_{out}(t)$  is alternating.

It turns out current sources are hard to implement.  
How can we force a constant current through a capacitor?

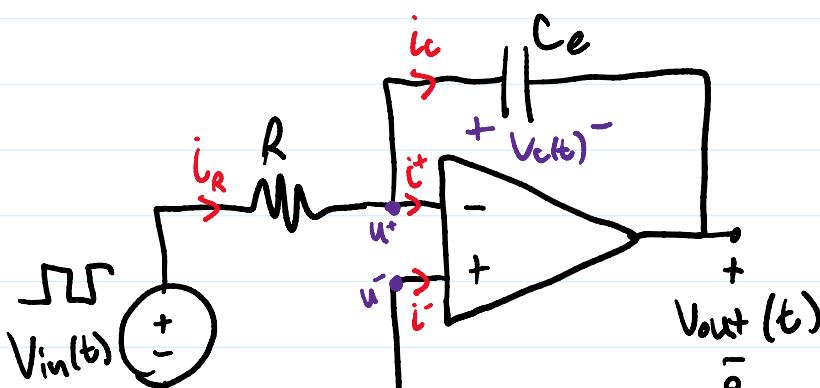Integrator circuit:  $V_{out}(t) = \int V_{in}(t) dt$



negative feedback? ✓

$$GR \#2: u^+ = u^- \rightarrow = 0$$

$$KCL @ u^+: GR \#1$$

$$i_R - i_c = 0$$

$$V_{in(t)}$$

$$V_{out}(t)$$

$$\frac{V_{out}(t)}{C_e}$$

$$i_R - i_L - i_C = 0$$

$$\frac{V_{in} - V_{out}}{R} - 0 - C_e \frac{\partial V_{out}}{\partial t} = 0$$

$$V_o = \cancel{V_{in}}^0 - V_{out}$$


$$= -V_{out}$$

$$\frac{V_{in}}{R} + C_e \frac{\partial V_{out}}{\partial t} = 0$$

$$V_{out}(t) = -\frac{1}{RC_e} \int V_{in}(t) dt$$

Connect output of Integrator to earlier comparator circuit  
 ~ Skipped a few steps but more explanation in Notes 2e  
 and Touch 3 lab

### Touch 3 (Lab) Final Circuit

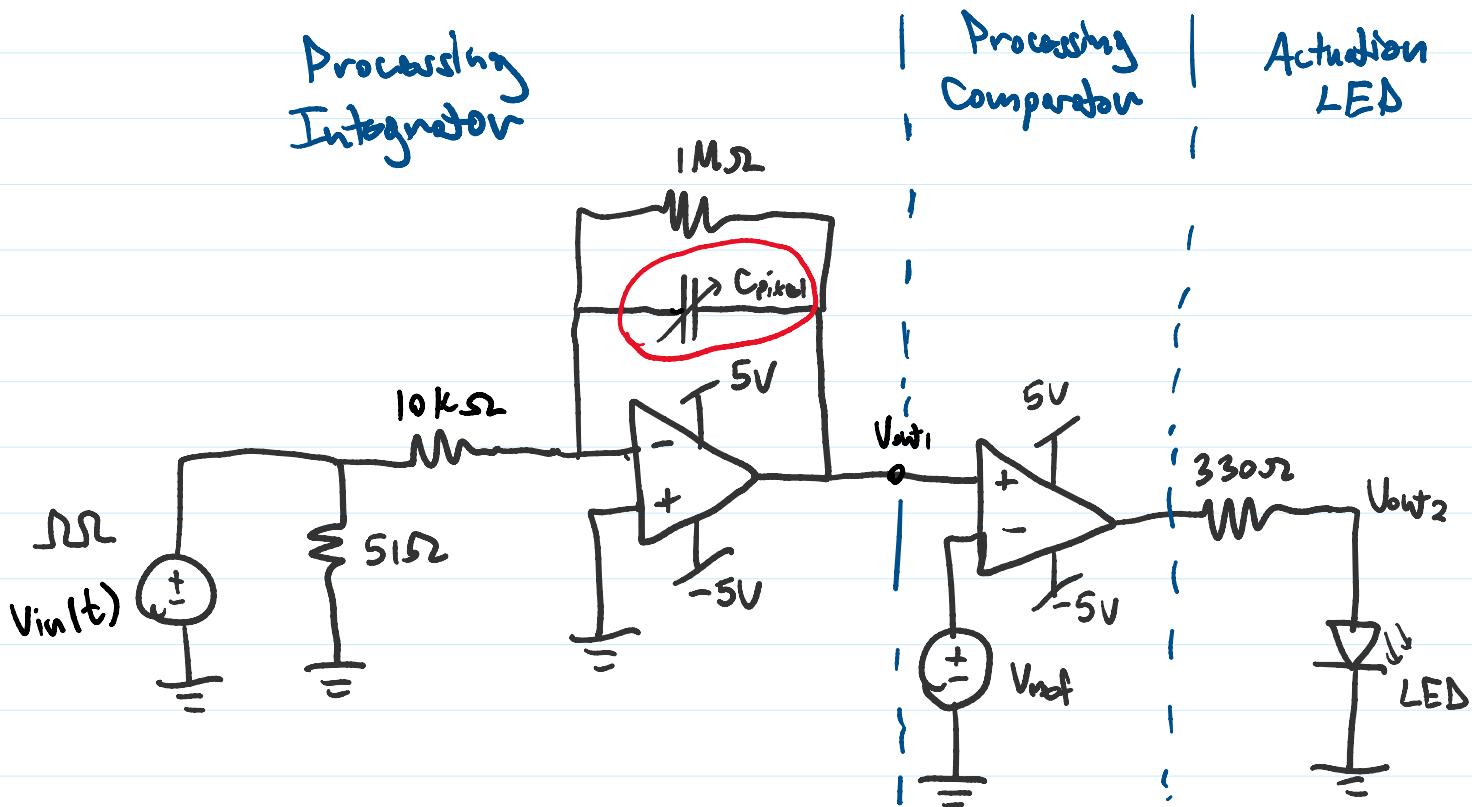

When touch,  $C_{pixel}$  increases and LED stops flashing

THE END (of Module #2)

Thank you! :)