

---

EECS 16A  
Summer 2023

Designing Information Devices and Systems I

Discussion 06A

---

**1. Dynamical Systems (Spring 2020 Midterm 1 Question 7)**

Define matrices  $Q, R \in \mathbb{R}^{2 \times 2}$  according to

$$Q = \begin{bmatrix} 0 & 3/4 \\ 1 & 1/4 \end{bmatrix}, \quad R = \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix}.$$

- (a) Find the eigenvalues for the matrix  $Q$ .

**Answer:** The eigenvalues are  $\lambda_1 = 1, \lambda_2 = -3/4$ .

- (b) Consider a system with state vector  $\vec{x}[n] \in \mathbb{R}^2$  at time  $n \geq 1$  given by


$$\vec{x}[n] = Q\vec{x}[n-1].$$

Is there a non-zero vector  $\vec{x}$  satisfying  $\vec{x} = Q\vec{x}$ ? If yes, give one such vector.

**Answer:** Yes;  $\vec{x} = [3/4, 1]^\top$ .

- (c) Draw the state-transition diagram for the system in part (b). Label your nodes "A" and "B".

**Answer:**

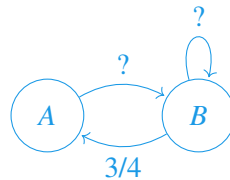

- (d) Now, consider a system with state vector  $\vec{w}[n] \in \mathbb{R}^2$  at time  $n \geq 1$  given by:

$$\vec{w}[n] = \begin{cases} Q\vec{w}[n-1] & \text{if } n \text{ is odd} \\ R\vec{w}[n-1] & \text{if } n \text{ is even.} \end{cases}$$

Write expressions for  $\vec{w}[1]$ ,  $\vec{w}[2]$ ,  $\vec{w}[3]$  and  $\vec{w}[4]$  in terms of  $\vec{w}[0]$  and  $Q$  and  $R$ . Write each answer in the form of a matrix-vector product.

**Answer:**

$$\vec{w}[1] = Q\vec{w}[0], \quad \vec{w}[2] = RQ\vec{w}[0], \quad \vec{w}[3] = Q(RQ)\vec{w}[0], \quad \vec{w}[4] = (RQ)^2\vec{w}[0].$$

- (e) Suppose we start the system of part (d) with state  $\vec{w}[0] = [11/14 \quad 3/14]^\top$ . Find expressions for  $\vec{w}_{\text{even}}$  and  $\vec{w}_{\text{odd}}$ , which are defined according to

$$\vec{w}_{\text{even}} = \lim_{k \rightarrow \infty} \vec{w}[2k], \quad \vec{w}_{\text{odd}} = \lim_{k \rightarrow \infty} \vec{w}[2k+1].$$


In words,  $\vec{w}_{\text{even}}$  and  $\vec{w}_{\text{odd}}$  describe the long-term behavior of the system at even and odd time-instants, respectively. (Hint: you can avoid computation by thinking about the system at even time-instants in terms of a state-transition diagram.)

**Answer:**

$$\vec{w}_{\text{even}} = \lim_{k \rightarrow \infty} \vec{w}[2k] = \begin{bmatrix} 1 \\ 0 \end{bmatrix}, \quad \text{and, } \vec{w}_{\text{odd}} = Q\vec{w}_{\text{even}} = \begin{bmatrix} 0 \\ 1 \end{bmatrix}.$$
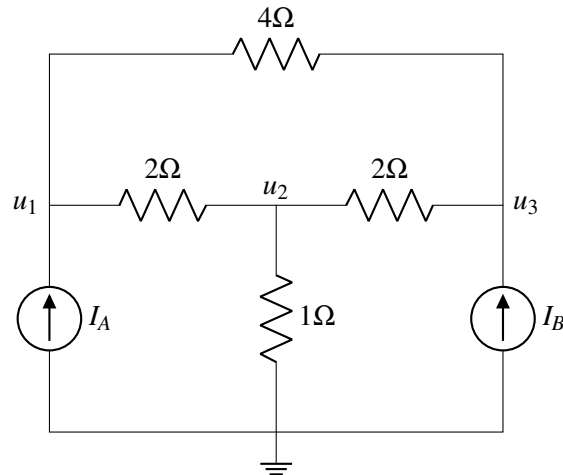
## 2. Superposition (Fall 2020 Midterm 2 Question 7)

For this question, we will analyze the circuit shown below with the two current sources of strength  $I_A$  and  $I_B$  as inputs. It may be observed that the network of resistors shown in the circuit is symmetric. We will first solve this circuit for symmetric inputs  $I_A = I_B$ , and then for anti-symmetric inputs  $I_A = -I_B$ . Using these two results, we we will solve the circuit for arbitrary inputs  $I_A, I_B$ .




- (a) Consider the circuit above with symmetric inputs,  $I_A = I_B = 1\text{A}$ . Using superposition, solve for the node voltages at the nodes marked  $u_1$ ,  $u_2$  and  $u_3$ .

- (b) Consider the same circuit as before with anti-symmetric inputs,  $I_A = 1\text{ A}$  and  $I_B = -1\text{ A}$ . Using superposition solve for the node voltages at the nodes marked  $u_1$ ,  $u_2$  and  $u_3$ .

### 3. Thévenin/Norton Equivalence

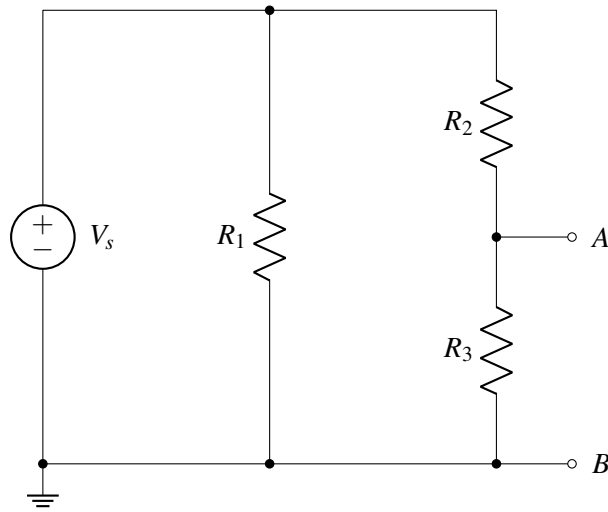- (a) Find the Thévenin resistance  $R_{th}$  of the circuit shown below, with respect to its terminals  $A$  and  $B$ .




**Answer:** To find the Thévenin resistance, we null out the voltage source (which shorts out  $R_1$ ) and find the equivalent resistance, which is:

$$R_{th} = R_2 \parallel R_3$$


since resistors  $R_2$  and  $R_3$  are in parallel.

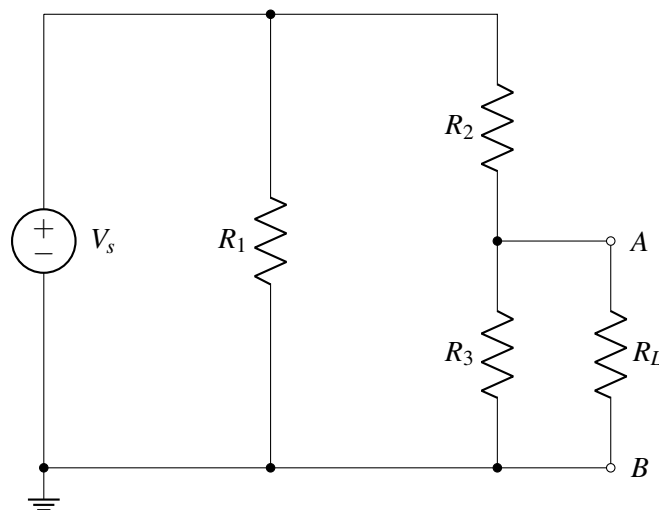- (b) Now a load resistor,  $R_L$ , is connected across terminals  $A$  and  $B$ , as shown in the circuit below. Using Thévenin equivalence, find the power dissipated in the load resistor in terms of the given variables.



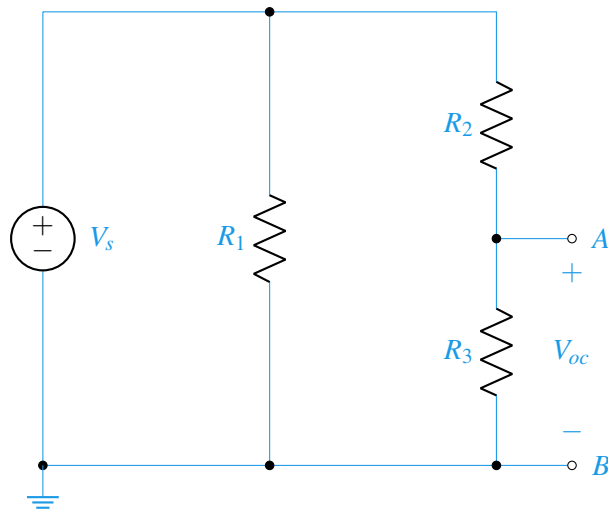**Answer:**

To help simplify the analysis, we replace the circuit with its Thévenin equivalent circuit. In order to do so, we first need to find the Thévenin voltage,  $V_{th}$ . One way to determine  $V_{th}$  is to find the open circuit voltage,  $V_{AB} = V_{oc}$ , in the original circuit when an open circuit is connected externally to terminals  $A$  and  $B$ .




The open circuit can be derived from a voltage divider:

$$V_{th} = V_{oc} = \frac{R_3}{R_2 + R_3} V_s$$

We also already know the Thévenin resistance  $R_{th} = R_2 \parallel R_3$  from part (a).

Thus, the circuit can be simplified to:

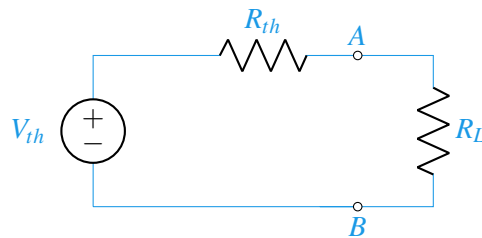


The power through the load resistor is then given by:


$$P_{R_L} = V_{R_L} \cdot I_{R_L} = I_{R_L}^2 \cdot R_L = \left( \frac{V_{th}}{R_L + R_{th}} \right)^2 R_L = \left( \frac{R_3}{R_2 + R_3} V_s \cdot \frac{1}{R_L + R_2 \parallel R_3} \right)^2 R_L$$
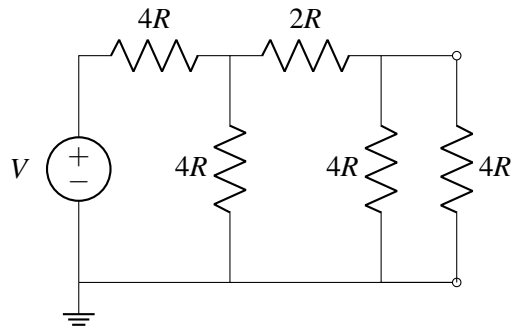
#### 4. OPTIONAL: Power to Resist ( from Spring 2018 midterm 2)

Find the power dissipated by the voltage source in the circuit below. Be sure to use passive sign convention.



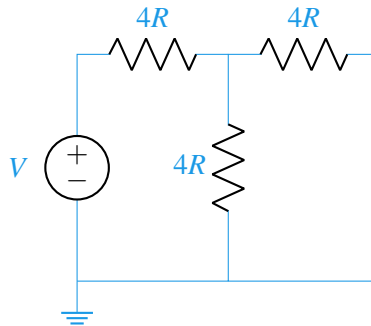**Answer:** We want to find the equivalent resistance across the voltage source in Figure 6.2. Start by reducing the two resistors on the right to  $4R \parallel 4R = 2R$ . Then combine the other  $2R$  resistor with this to get a new resistor of value  $4R$  as in the circuit below.



Once again we have  $4R \parallel 4R = 2R$ . This is finally in series with  $4R$  giving us a total resistance of  $4R + 2R = 6R$

$$P = VI = V \frac{-V}{6R} = -\frac{V^2}{6R}$$

The negative sign is present because the voltage source actually provides power, which can also be seen by using passive sign convention.