

Lecture 5C: (7/19/23)


Announcements:

- Quest Grade Request due tonight
- Today's content (including discussion) is end of scope for the Midterm (Monday night!)


Today's Topics:

- Capacitors (Note 1b)
 - IV Characteristics
 - Capacitor Circuits and Charge Sharing
 - Capacitor Equivalence
 - Physical Capacitors


Consider yesterday's circuit

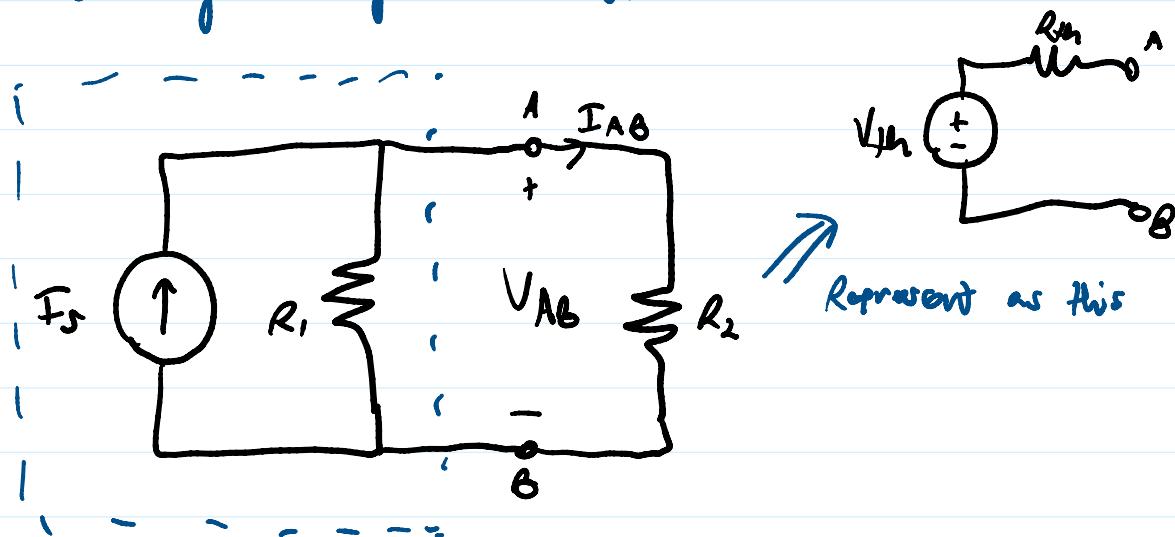

open-circuit test:
(measures V_{AB})

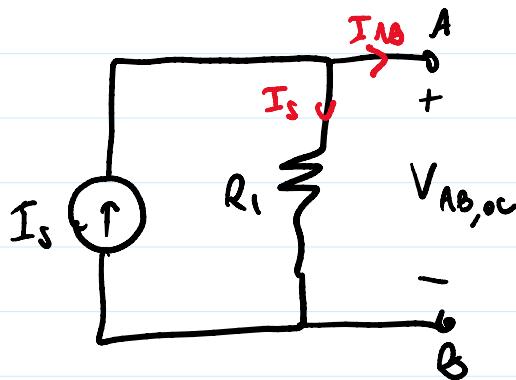

short-circuit test:
(measures I_{AB})

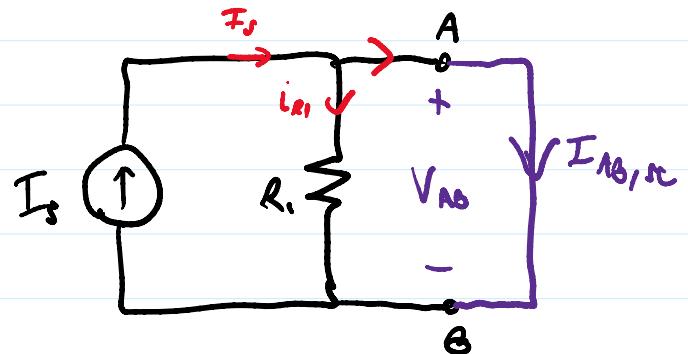



$$V_{AB} = 0 \rightarrow I_{R_1} = 0$$

$$V_{th} = V_{AB,oc} = I_s R_1$$


$$I_{no} = I_{AB,sc} = I_s$$

$$R_{th} = \frac{V_{th}}{I_{no}} = \frac{I_s R_1}{I_s} = R_1$$


Result:

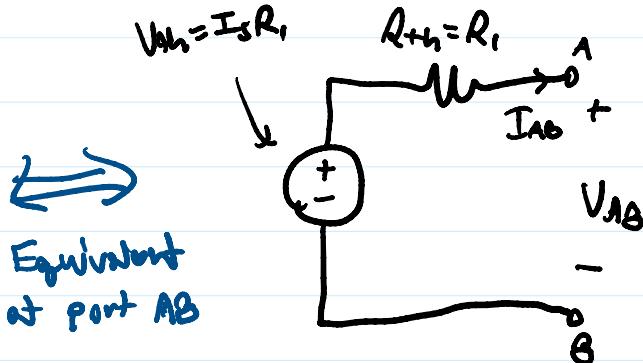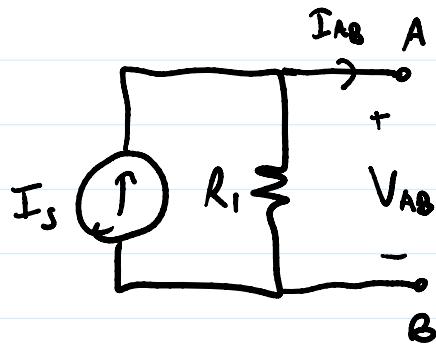


Thévenin equivalent circuit:

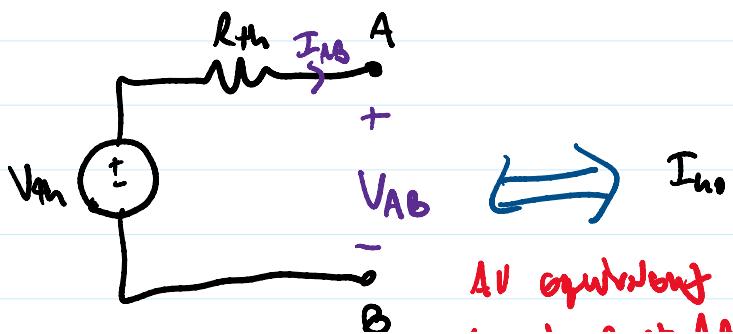



Norton equivalent circuit

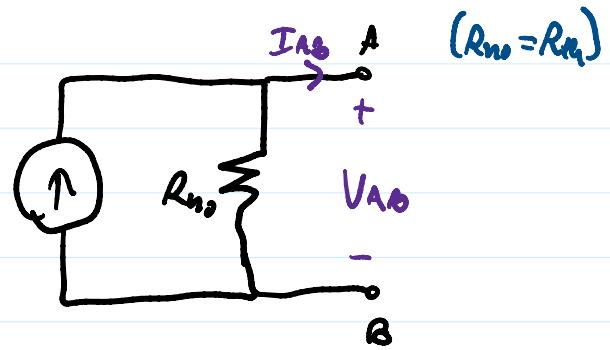

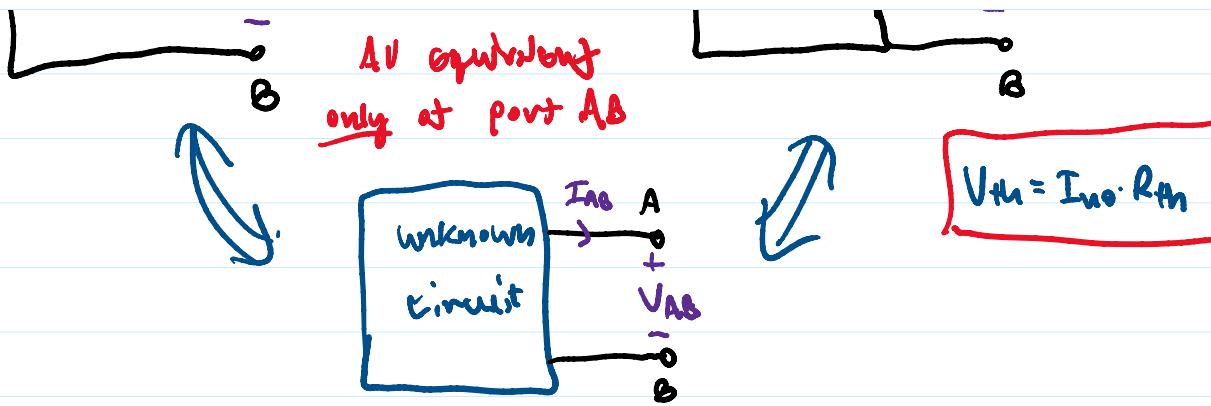


Another method to find R_{th} :

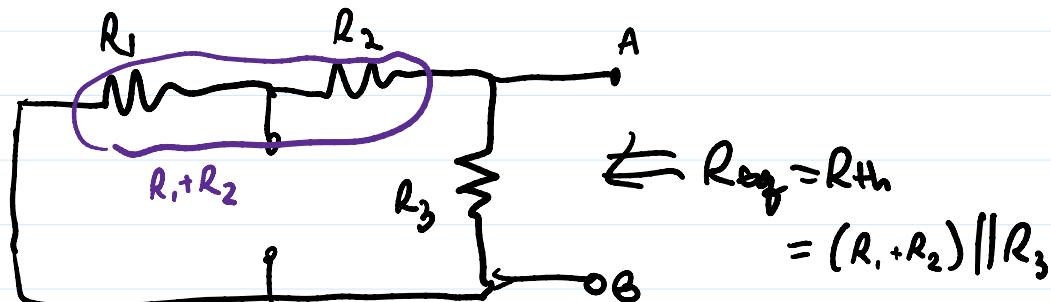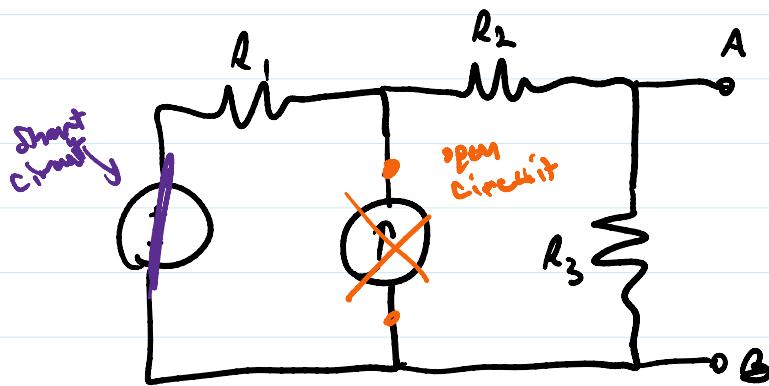- * Turn off all independent voltage and current sources and find equivalent resistance between A and B



What is a capacitor?

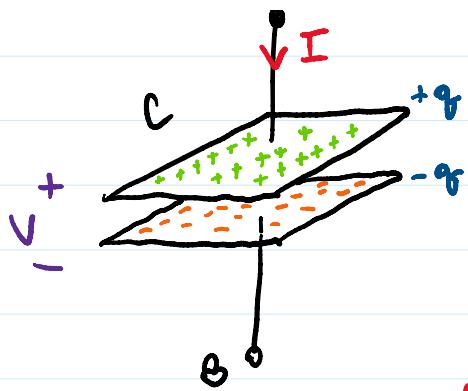 A capacitor...
+q - stores and releases energy / does not dissipate energy




A capacitor...

- Stores and releases energy (does not dissipate energy like a resistor)
- Separates charges
- Has capacitance variable: "C" unit: [F] (Farad)
- Has a linear IV characteristic


How is
this an "IV"
characteristic?

$$q = CV \quad \begin{matrix} \uparrow \\ \text{charge} \end{matrix} \quad \begin{matrix} \uparrow \\ \text{capacitance} \end{matrix} \quad \begin{matrix} \rightarrow \\ \text{Voltage [V]} \end{matrix}$$

Resistor:

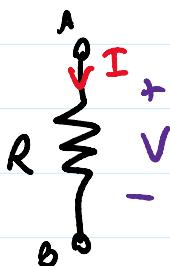

$$V = IR$$

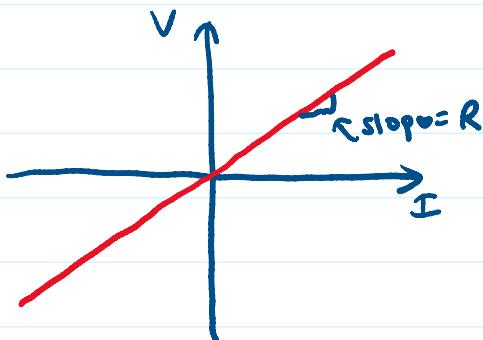


Capacitor:



$$q = CV$$

$$\frac{\partial}{\partial t} q = \frac{\partial}{\partial t} (CV)$$

$$I = C \frac{\partial V}{\partial t}$$

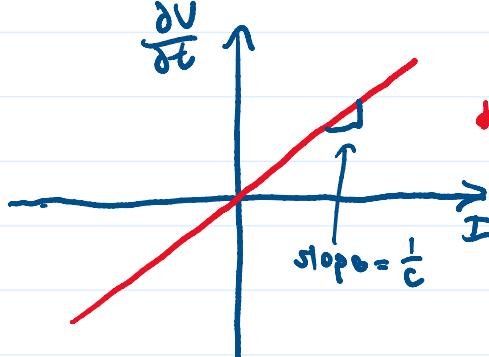

A capacitor is a linear passive circuit element
 → many of our linear circuit analysis techniques apply

Ex). Find V_c




$$q = CV_c \rightarrow I_c = C \frac{\partial V_c}{\partial t}$$

$I_c = I_s$ constant

$$\int_{t_0}^t I_c dt = \int_{V_c(t_0)}^{V_c(t)} C dV_c$$

C is constant

Separate and integrate!

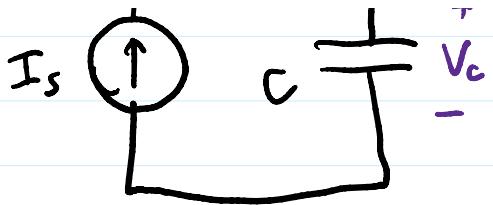

$$\int_{t_0}^t \frac{dV_c}{dt} dt = I_s \cdot \Delta V_c$$

$$I_s \cdot t \Big|_{t_0}^t = C \cdot V_c(t) \Big|_{V_c(t_0)}$$

$$I_s \cdot t - I_s \cdot t_0 = C \cdot V_c(t) - C \cdot V_c(t_0)$$


$$V_c(t) = \frac{1}{C} I_s \cdot (t - t_0) + V_c(t_0)$$

What if we know $I_s = 1A$, $C = 0.5 F$
and $V_c(t_0) = 2V$ at time $t_0 = 0 s$?


$$V_c(t) = \frac{1}{(0.5F)} \cdot (1A) \cdot (t - 0) + (2V)$$

$$= (2 \frac{V}{s}) \cdot t + 2V$$

\uparrow
volt per second

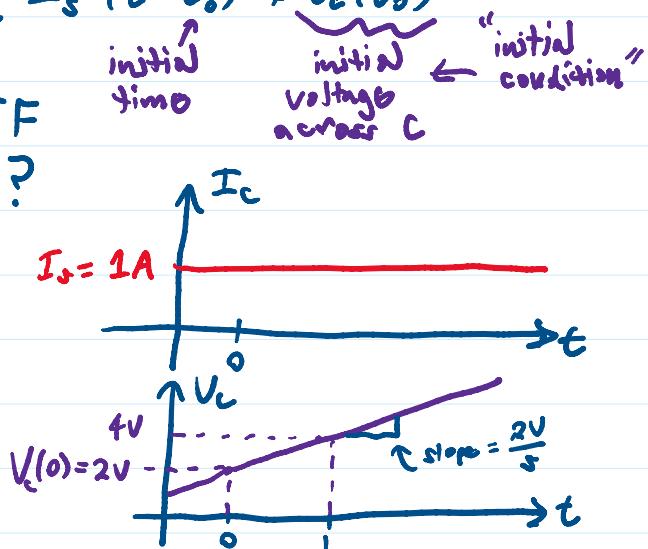

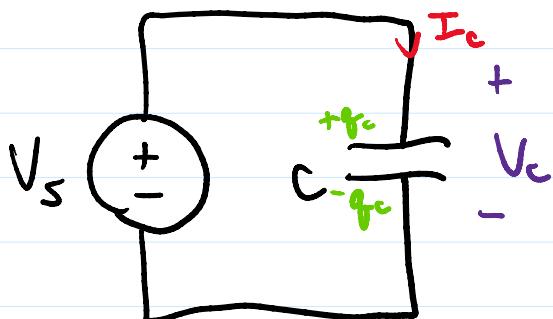Ex). Find charge across the capacitor, q_c



$$q_c = C V_c = C V_s$$


capacitor voltage is static (i.e., constant) with time

What about current through the capacitor, I_c ?

Capacitor has nonzero charge and voltage across it, but no current flowing through it.

$$I_c = C \frac{\partial V_c}{\partial t} = C \cdot 0 = 0 A$$

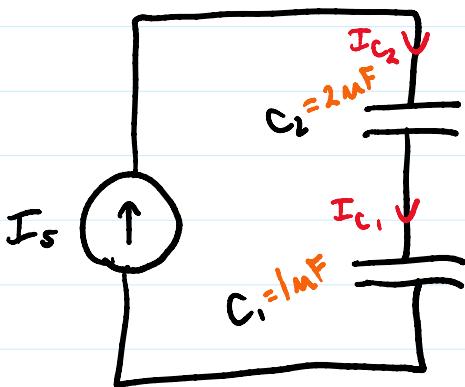Ex.). Capacitors in series. Find V_{C1} . Assume $V_{C1}(0) = V_{C2}(0) = 0V$



$$+ \\ V_{C2} = 2V_{C1} \\ -$$

$$I_{C1} = I_{C2} = I_s$$

$$I_c = C \frac{dV_c}{dt}$$

$$C_1 \frac{dV_{C1}}{dt} = C_2 \frac{dV_{C2}}{dt} = I_s$$

$$C_1 \int_{V_{C1}(t_0)}^{V_{C1}(t)} dV_{C1} = C_2 \int_{V_{C2}(t_0)}^{V_{C2}(t)} dV_{C2} = I_s \int_{t_0}^t dt$$

$$C_1 V_{C1}(t) - C_1 V_{C1}(t_0) = C_2 V_{C2}(t) - C_2 V_{C2}(t_0) = I_s \cdot (t - t_0)$$

$$C_1 V_{C1}(t) = C_2 V_{C2}(t) = I_s t$$

Pick $t_0 = 0$

The accumulated charge in series capacitors is equal since they share the same current $I = \frac{dq}{dt}$.


However, they have different voltages

$$\{ q_{C1}(t) = q_{C2}(t) = I_s t$$

Pick $C_1 = 1mF$, $C_2 = 2mF$, then $V_{C2}(t) = \frac{C_2}{C_1} \cdot V_{C1}(t) = 2 \cdot V_{C1}(t)$

Equivalent Capacitance

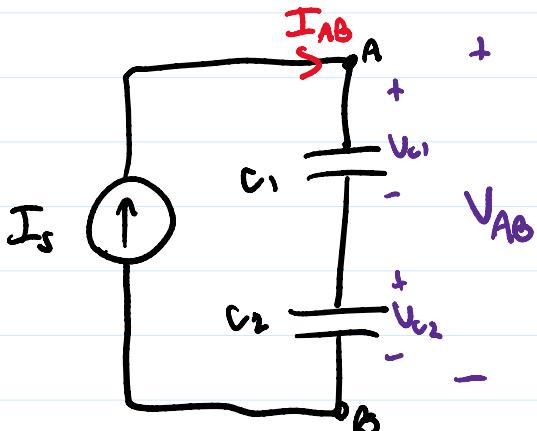
Series Capacitors \leftarrow Share the same current



$$V_{AB} = V_{C1} + V_{C2}$$

$$\frac{\partial V_{AB}}{\partial t} = \frac{\partial V_{C1}}{\partial t} + \frac{\partial V_{C2}}{\partial t} \quad I_{C1} = I_{C2} = I_{AB}$$

Equivalent

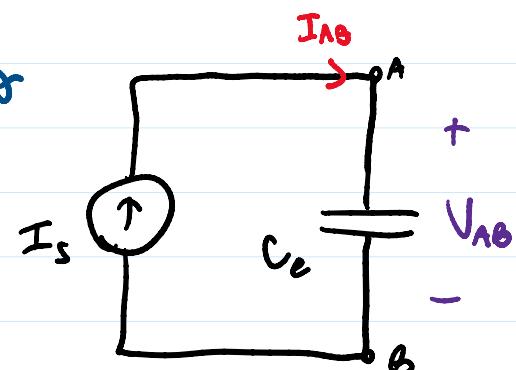

$$V_{AB} \rightarrow \frac{\partial V_{AB}}{\partial t}$$

$$\Delta V_{AB} = \frac{1}{C_e} + \frac{1}{t}$$

$$\frac{\partial V_{AB}}{\partial t} = \frac{\partial V_{C1}}{\partial t} + \frac{\partial V_{C2}}{\partial t}$$

$$I_{C1} = I_{C2} = I_{AB}$$

$$= \frac{1}{C_1} I_{C1} + \frac{1}{C_2} I_{C2} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right) I_{AB}$$

$$I_{AB} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1} \cdot \frac{\partial V_{AB}}{\partial t}$$


$C_e = C_1 \parallel C_2 = \frac{C_1 C_2}{C_1 + C_2}$

Equivalent
parallel operator
for series capacitors

$$\frac{\partial V_{AB}}{\partial t} = \frac{1}{C_e} I_{AB}$$

$$I_{AB} = C_e \cdot \frac{\partial V_{AB}}{\partial t}$$

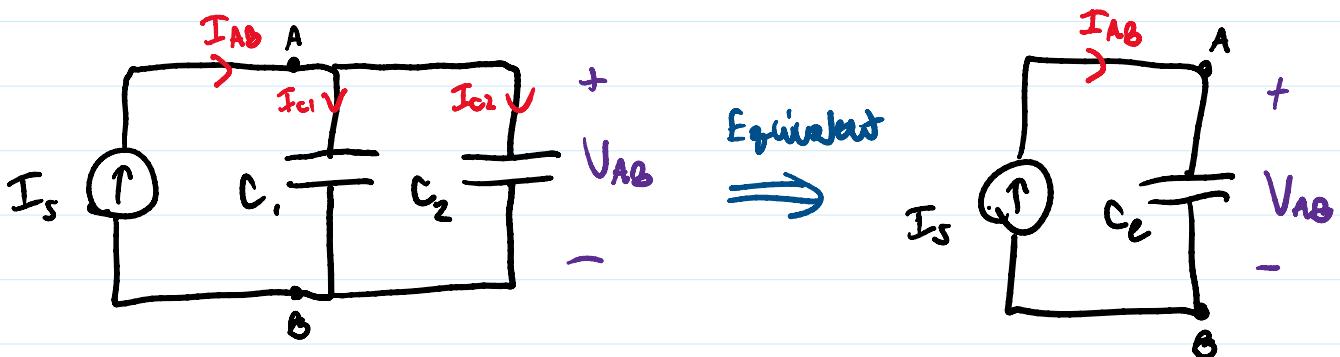Parallel Capacitors \leftarrow share the same voltage



$$I_{AB} = I_{C1} + I_{C2} \quad (\text{KCL})$$

$$= C_1 \frac{\partial V_{C1}}{\partial t} + C_2 \frac{\partial V_{C2}}{\partial t}$$

$$I_{AB} = C_e \cdot \frac{\partial V_{AB}}{\partial t}$$

$$I_{AB} = (C_1 + C_2) \cdot \frac{\partial V_{AB}}{\partial t}$$


$C_e = C_1 + C_2$

$V_{AB} = V_{C1} = V_{C2}$

$$\frac{\partial V_{AB}}{\partial t} = \frac{\partial V_{C1}}{\partial t} = \frac{\partial V_{C2}}{\partial t}$$

"series" operator
for parallel capacitors

Physical Capacitor:

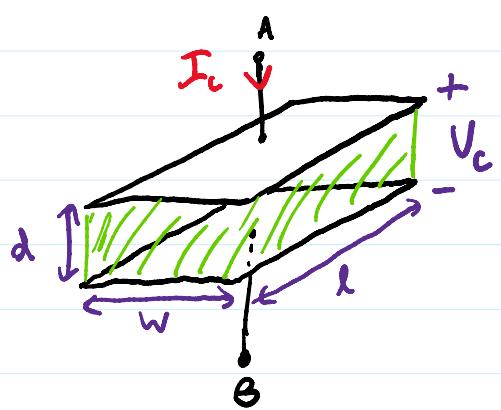

Capacitance forms between overlapping parallel plates of metal.

$$C = \epsilon \frac{A}{d}$$

permittivity

overlapping plate area

plate separation distance

$$= \epsilon \frac{l \cdot w}{d}$$

for this example

$$[F] = \left[\frac{F}{m} \right] \cdot \frac{[m^2]}{[m]}$$

What is permittivity?

- Intrinsic material property
- Variable " ϵ " (Greek letter "Epsilon")
- Often expressed as: $\epsilon = \epsilon_r \cdot \epsilon_0$ ← "permittivity of free space" (vacuum) or air
- Dielectric material has $\epsilon_r > 1$

$$\epsilon_0 = 8.85 \cdot 10^{-12} \frac{F}{m}$$

\uparrow
relative permittivity

Demo with copper plates:

Two 15×15 cm plates held 1 cm apart in air

$$C = \epsilon \cdot \frac{l \cdot w}{d} = \frac{(15\text{cm}) \cdot (15\text{cm})}{(1\text{cm})} = (8.85 \cdot 10^{-12} \frac{F}{m}) \cdot \frac{(0.15\text{m})^2}{(0.01\text{m})}$$

\uparrow
 $\epsilon \approx \epsilon_0$
for air

$$= 1.99 \cdot 10^{-11} \text{ F}$$

$$= 19.9 \text{ pF} \quad \text{Really small!}$$

What if area doubles? $\rightarrow C$ doubles

What if separation doubles? $\rightarrow C$ halves