

Lecture 5A: (7/17/23)


Announcements:

- Quest: grades are released. Mean: 82.1% Median: 87.3%
- You have until Wednesday at midnight to request a regrade
- Midterm: Next Monday from 5-7pm, Dwinelle 145
- Lab - Touch 1 (Tues) and Touch 2 (Thurs)
 - Please consider moving sections
- Office Hours - Mon/Wed 1-2pm in Cory 144MA
HW Party - Friday 10am-noon ↴
- Today's Topics:
 - Voltage/Current Measurement (Note 13)
 - 1D Resistive Touchscreen (Note 13)
 - 2D Resistive Touchscreen (Note 14)
 - Superposition (Note 15)


Measuring Voltage and Current

Voltmeter: device which measures voltage across it

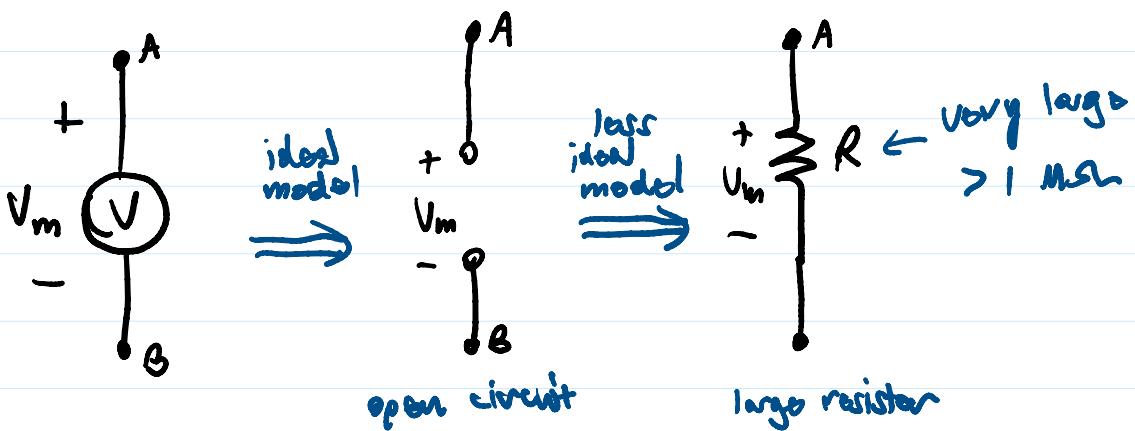Voltmeter: device which measures voltage across it




Ex).

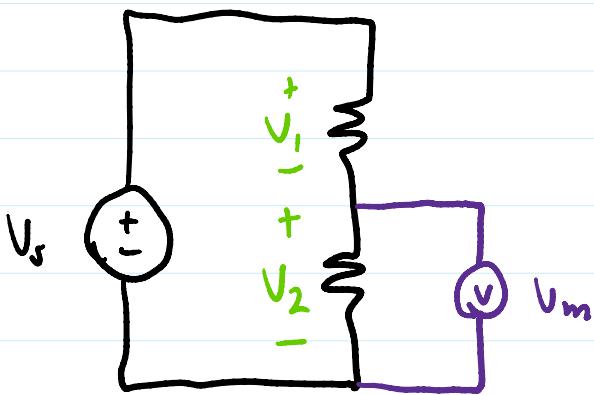

$$V_m = V_2$$

If voltmeter is open circuit then
 $P = V \cdot I = 0$ ↗
 no energy loss

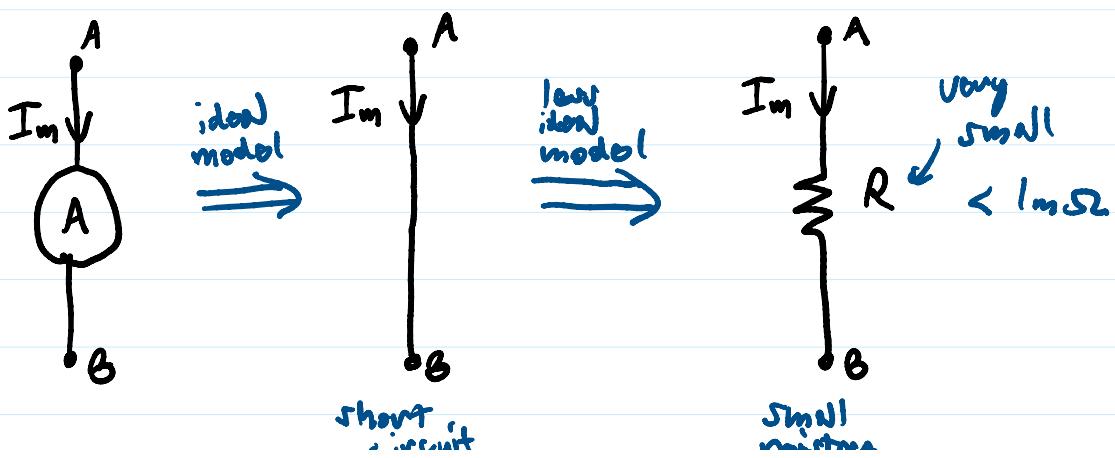ammeter: device which measures current (amp) through it



• B


• B

• B

short
circuit

short
circuit

Ex).

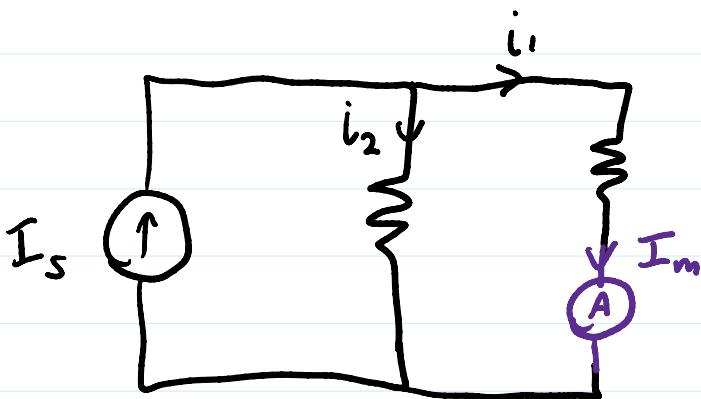


$$I_m = i_1$$


If unmotor is
short circuit, then

$$\rho = V \cdot i = 0 \text{ J} \\ = 0 \text{ no energy loss}$$

1D Resistive Touch

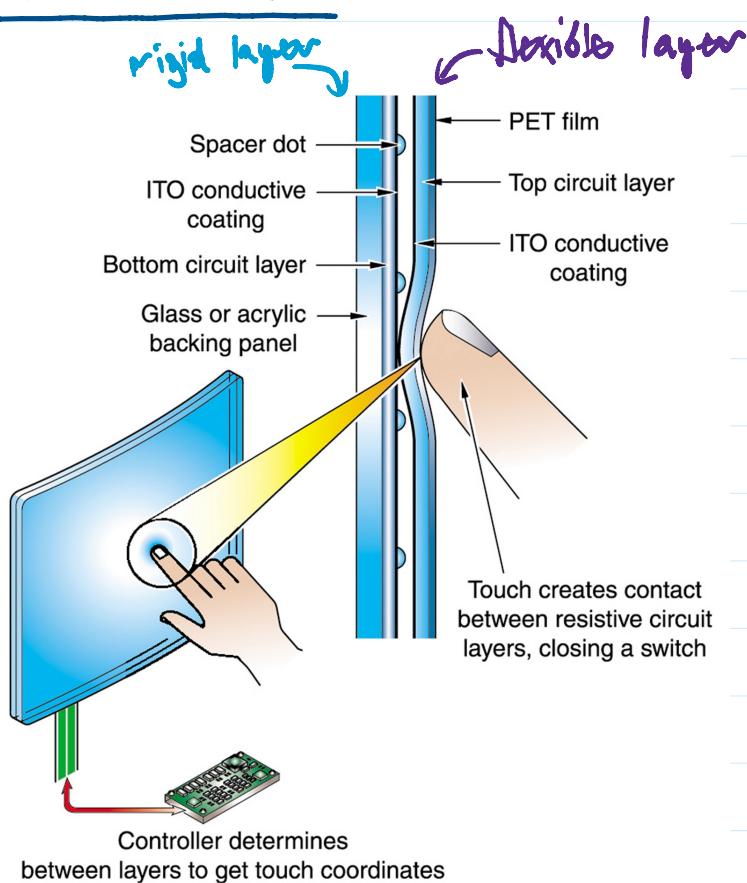

Both layers are
resistive!

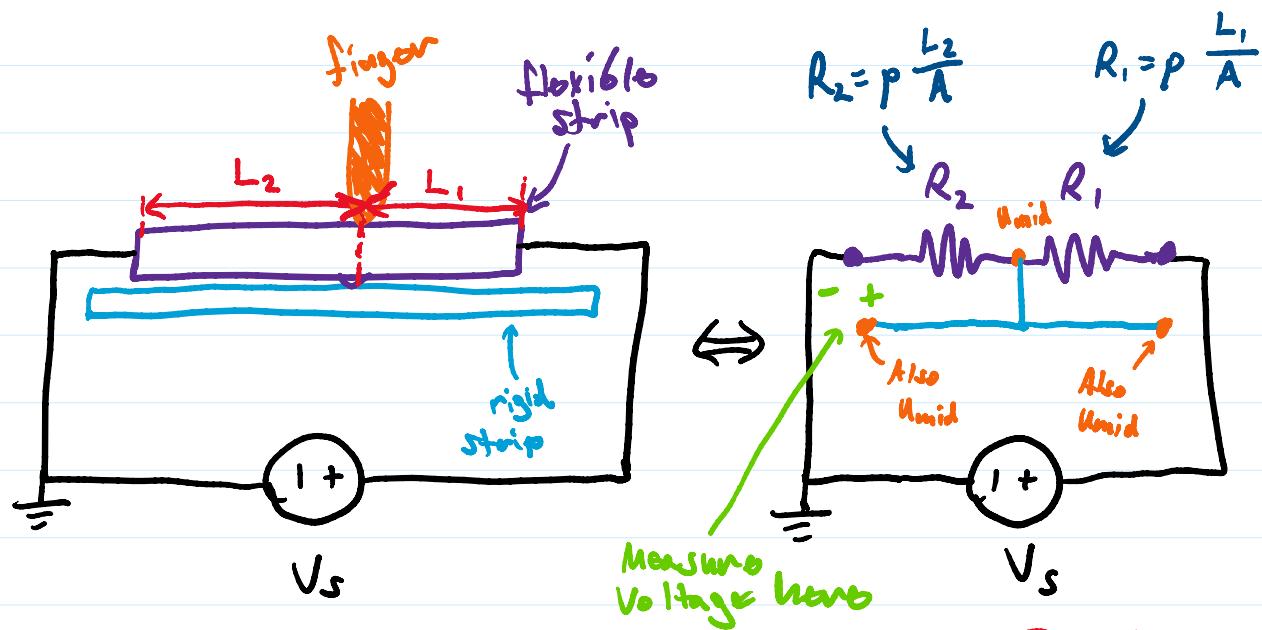


$$V_{mid} = \frac{R_2}{R_1 + R_2} V_s = \frac{\left(\rho \frac{L_2}{A}\right)}{\left(\rho \frac{L_1}{A}\right) + \left(\rho \frac{L_2}{A}\right)} V_s = \frac{L_2}{L_1 + L_2} V_s = \frac{L_2}{L_{total}} V_s$$

relative position

How can we actually measure V_{mid} ?

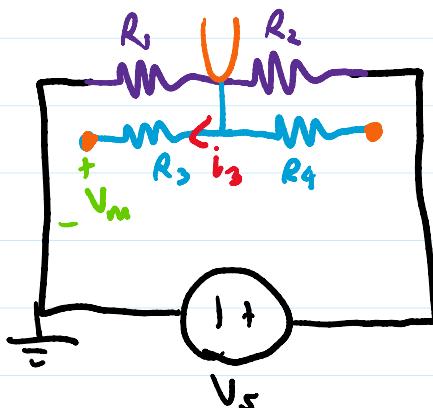Use rigid layer ← Doesn't this have resistance too? !!




Does measured V_m change because of R_3 and R_4 ?

How much current flows through R_3 ? $i_3 = 0$!

Current flow requires closed loops

The resistance of the rigid layer is inconsequential


Ex).

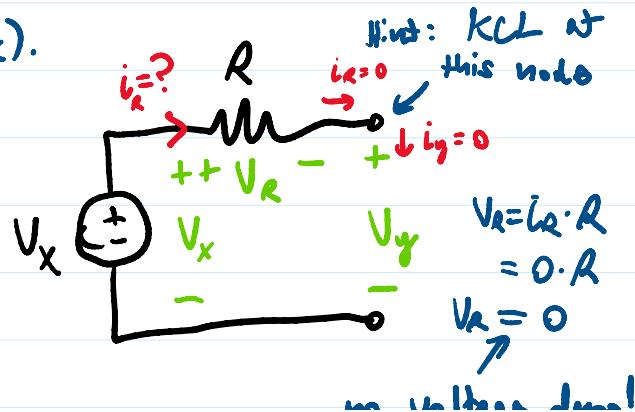

rigid layer is inconsequential

$$v_R = v \rightarrow \text{no voltage drop!}$$

Interesting Circuit:

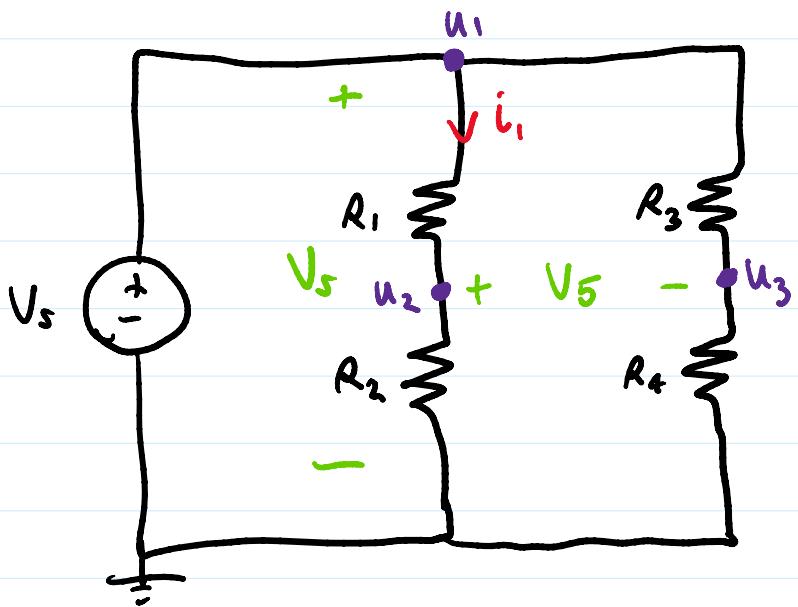

What is u_2 ?

$$u_2 = \frac{R_2}{R_1 + R_2} V_s$$

Add second branch:

What is u_3 ?

$$u_3 = \frac{R_4}{R_3 + R_4} V_s$$


Does u_2 change?
(Does i_1 change?)

No

$$i_1 = \frac{V_s}{R_1 + R_2} \quad u_2 = i_1 \cdot R_2 = \frac{R_2}{R_1 + R_2} V_s$$

If you add (or subtract) to the circuit, the circuit voltages and currents likely change. \leftarrow Need to check

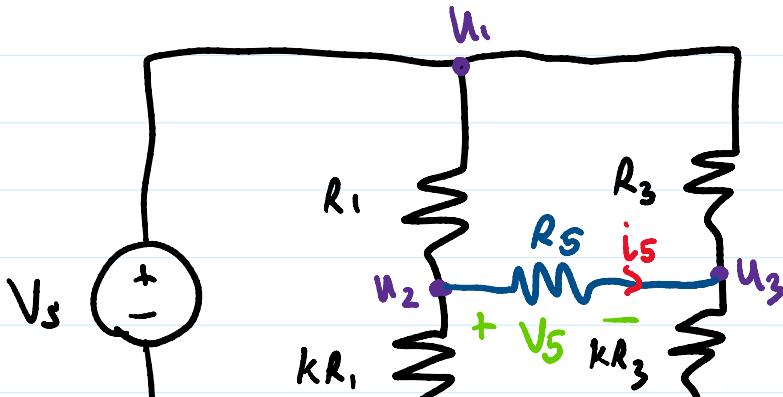
What if $R_2 = k \cdot R_1$ and $R_4 = k \cdot R_3$?



$$u_2 = \frac{kR_1}{kR_1 + R_2} V_s = \frac{k}{1+k} V_s$$

$$u_3 = \frac{kR_3}{R_3 + kR_3} V_s = \frac{k}{1+k} V_s$$

The same!

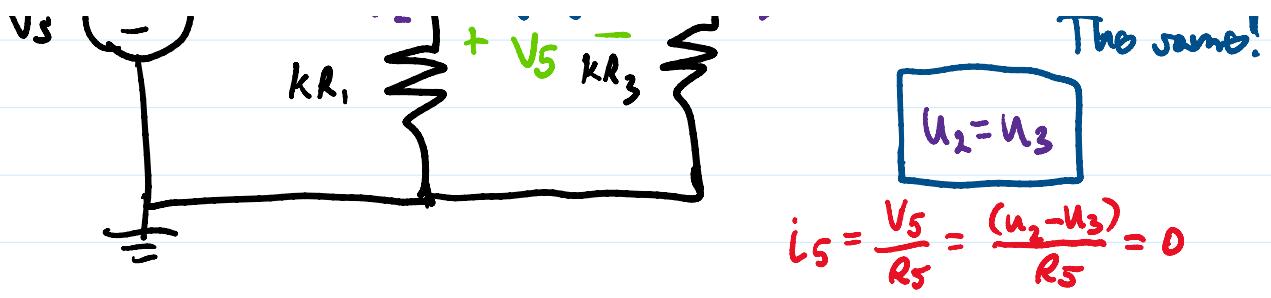

Let's add a resistor R_5 between u_2 and u_3 .

What's the current through this resistor?

Foolproof way \Rightarrow Perform full NVA

Sneaky way \Rightarrow Do u_2 and u_3 change?

Before:

$$V_5 = u_2 - u_3 = 0$$

After:


$$V_5 = u_2 - u_3 = 0$$


Trick: If you connect a resistor between two nodes with the same voltage, then it does not change the circuit \leftarrow "virtual open circuit"

since $i=0$ ALWAYS

I-V characteristic
of open circuit

2D Resistive Touch

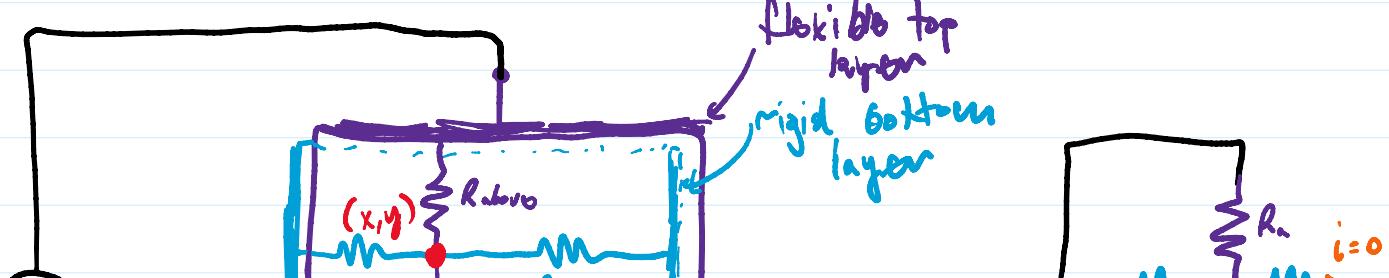

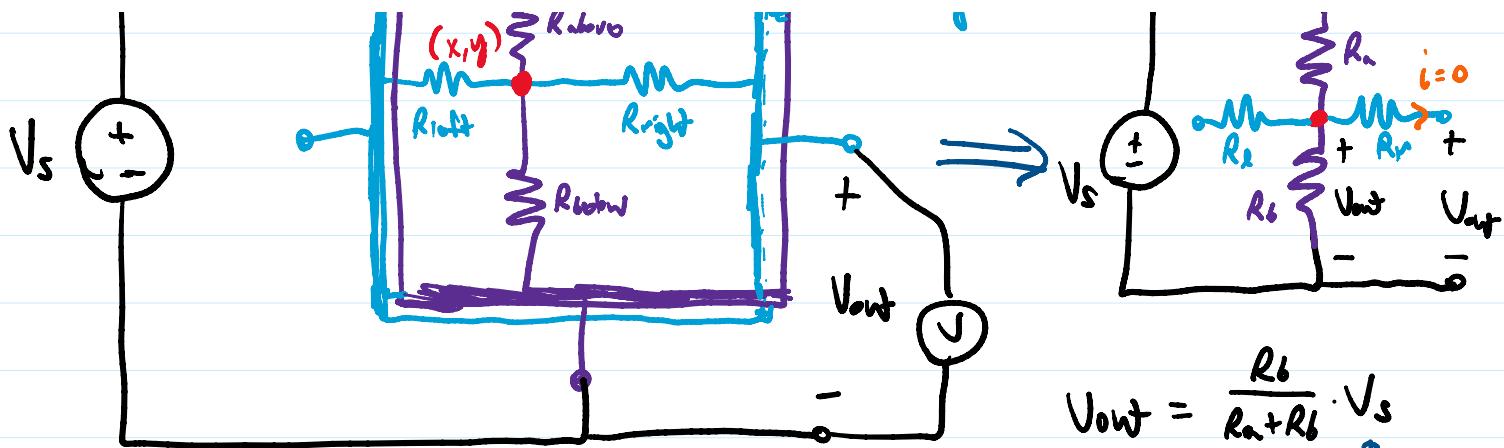



$$V_{out} = \frac{R_b}{R_a + R_b} \cdot V_s$$

↑ known ↑ known
 can determine y value

This circuit measures vertical position.

How can we measure horizontal position?

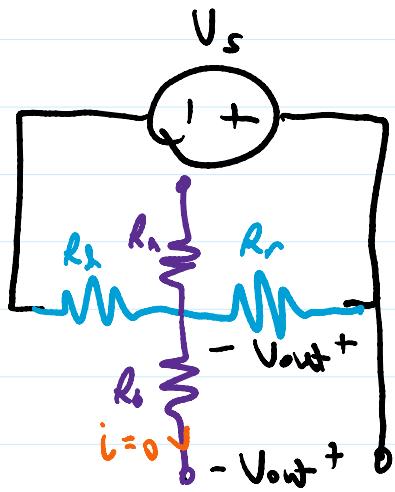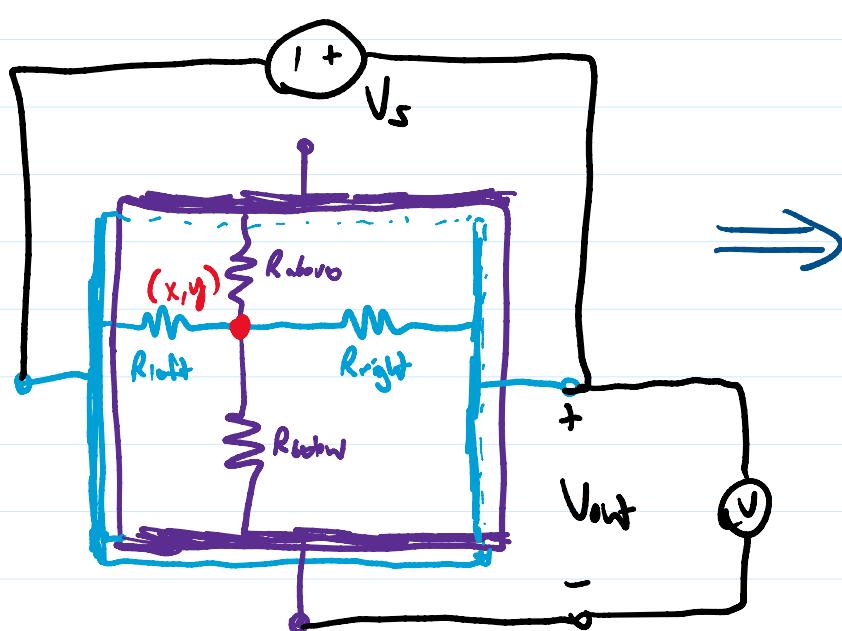- Connect voltage source to bottom layer.



$$V_{out}^+ = \frac{R_r}{R_l + R_r} \cdot V_s$$

This circuit measures horizontal position

Switch between two circuits to get both x and y .