

Lecture 5B: (7/18/23)Announcements:

- Lab - Touch 1


Today's Topics:

- Superposition
 - Circuit Equivalence
 - Equivalent Resistance
 - Thevenin/Norton Equivalents
- Note 15

Superposition

NVA always works, however can we linearly decompose a circuit into simpler circuits? YES!

Ex). Connecting two batteries

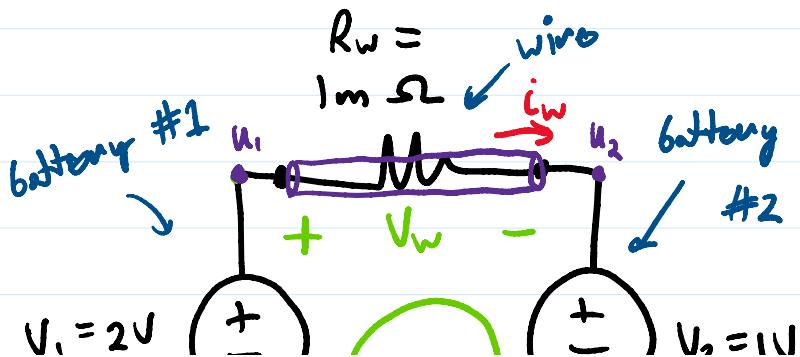


What's the current i_w through the wire?

Option 1: NVA

$$U_1 = 2V \quad U_2 = 1V$$

$$i_w = \frac{U_1 - U_2}{R_w} = 1000A$$

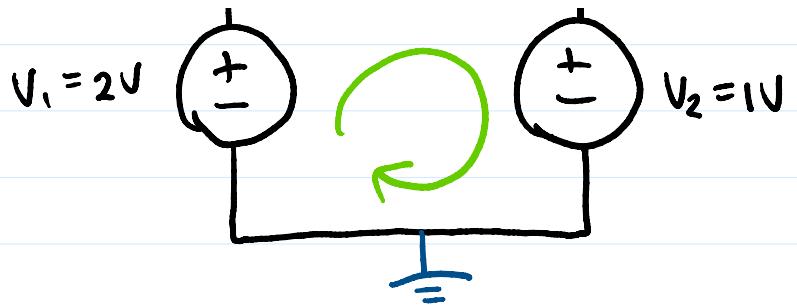

$$U_1 = 2V \quad U_2 = 1V$$

$$i_w = \frac{U_1 - U_2}{R_w} = 1000A$$


Option 2: KVL

$$2V - V_w - 1V = 0$$


$$V_w = 1V$$

$$i_w = \frac{V_w}{R_w} = 1000A$$

This much current would melt the wire

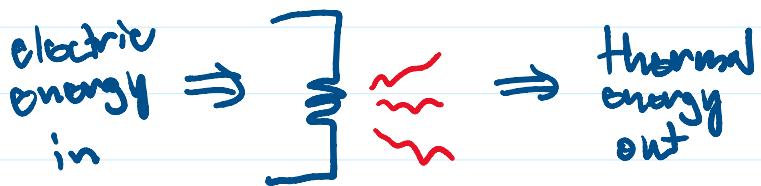

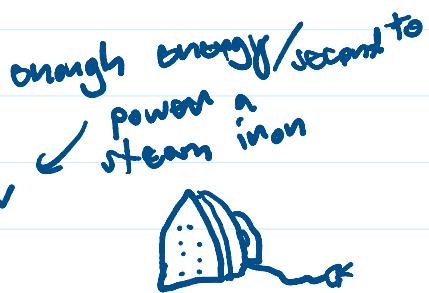
$$\text{power: } P = V_w \cdot i_w = (1V)(1000A) = 1000W$$




Maybe we shouldn't connect two batteries together with a wire...

Back to superposition
→ what if we "nullified" one of the voltage sources?

Null V_2

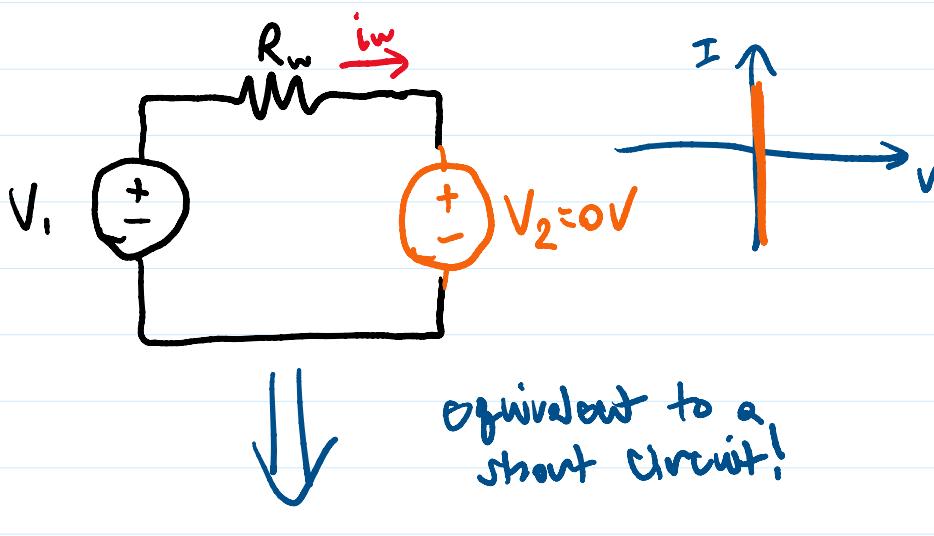


Null V_1

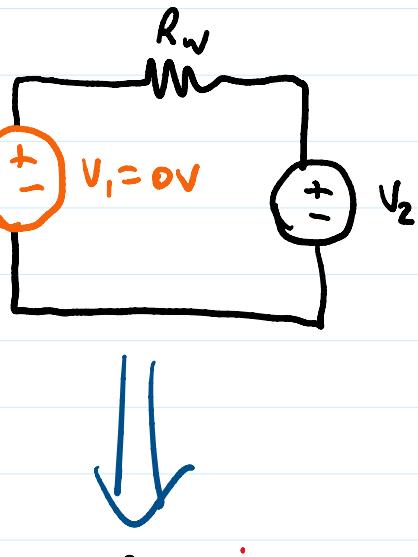


V

short circuit.

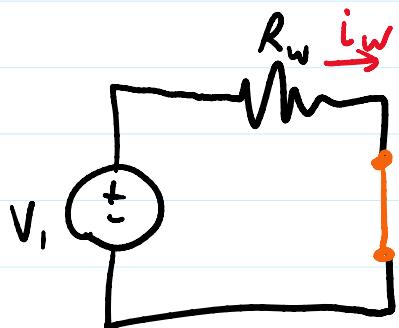

$$i_w|_{V_2=0} = \frac{V_1}{R_w}$$

V

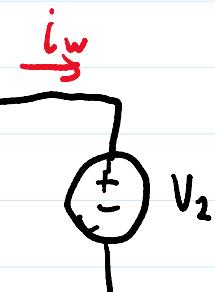

$$i_w|_{V_1=0} = -\frac{V_2}{R_w}$$

What if?

$$i_w = i_w|_{V_2=0} + i_w|_{V_1=0}$$

$$= \frac{V_1}{R_w} - \frac{V_2}{R_w} = \frac{2V}{1m\Omega} - \frac{1V}{1m\Omega} = 2000A - 1000A$$

$$= 1000A \leftarrow \text{same as before!}$$

This is superposition! Application of the same linearity property from Modulo #1

$$f(x+y) = f(x) + f(y)$$

$f(\cdot)$ is our LINEAR circuit

$$f(\vec{x}) = \vec{b}$$

linear

$$A\vec{x} = \vec{b}$$

write solution

$$\vec{x} = A^{-1}\vec{b}$$

node voltages

$$\begin{bmatrix} U_1 \\ U_2 \\ \vdots \\ U_n \end{bmatrix}$$

voltage/current sources


$$\begin{bmatrix} I_{S1} \\ I_{S2} \\ \vdots \\ V_{S1} \end{bmatrix}$$

Node voltage is linear combination of sources

↓


$$U_1 = \alpha_1 I_{S1} + \beta_1 I_{S2} + \gamma_1 V_{S1} + \dots$$

What about nulling current sources?

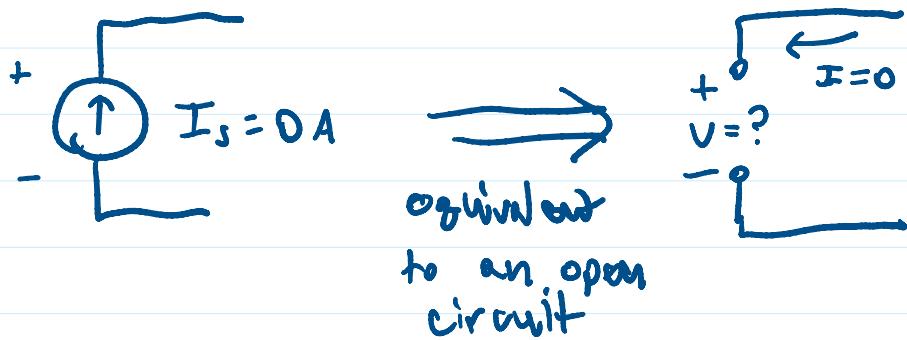

Circuit Equivalence:

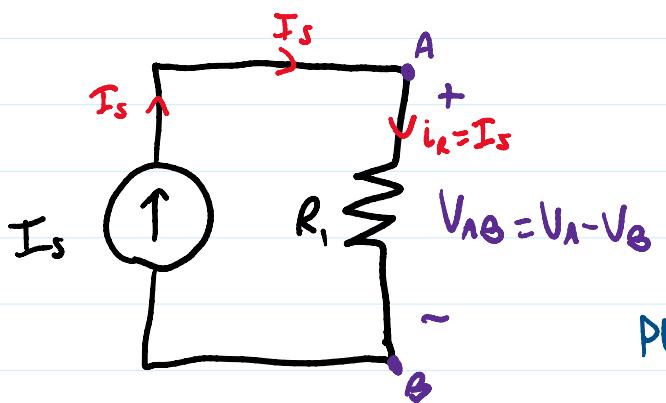We have a circuit and we want to connect another resistor to it \leftarrow connect to two nodes A, B




$$i_R = I_s \quad \curvearrowright$$

$$V_{AB} = i_R \cdot R_1 = I_s \cdot R_1 = 3V$$

Plug in some values! $I_s = 3A$ $R_1 = 1\Omega$

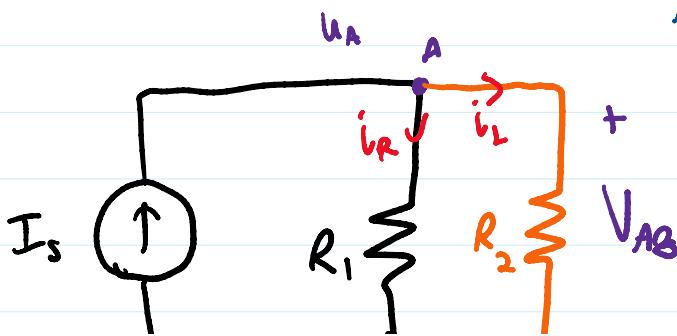Does V_{AB} change when we add resistor R_2 between nodes A and B?




Apply NVA:

$$\text{KCL @ A: } I_s - i_R - i_L = 0$$

$$I_s - \frac{u_A}{R_1} - \frac{u_A}{R_2} = 0$$
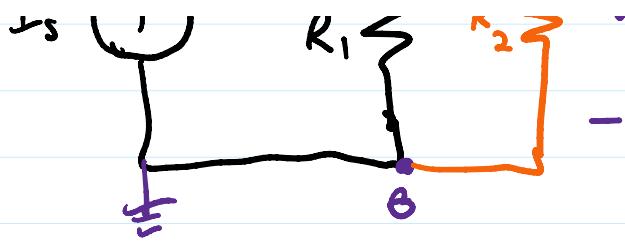
$$\text{Simplify: } I_s - \left(\frac{1}{R_1} + \frac{1}{R_2} \right) \cdot u_A = 0$$



$$\text{Simplify: } I_s - \left(\frac{1}{R_1} + \frac{1}{R_2}\right) \cdot U_A = 0$$

$$U_A = I_s \cdot \left(\frac{1}{R_1} + \frac{1}{R_2}\right)^{-1}$$

$$\rightarrow U_A = 3 \cdot \left(\frac{1}{1} + \frac{1}{2}\right)^{-1} = 3 \cdot \frac{2}{3} = 2V$$


The voltage decreased from 3V to 2V after adding R_2

Plug in some numbers!

$$\begin{aligned} I_s &= 3A \\ R_1 &= 1\Omega \\ R_2 &= 2\Omega \end{aligned}$$

Can this circuit be equivalently represented with other circuits?

Equivalent Resistance

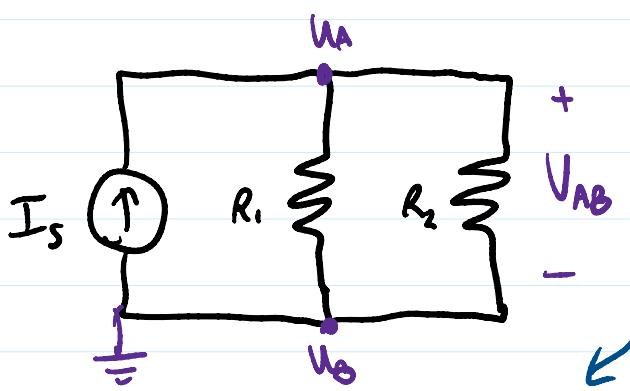


$$U_A - U_B = V_{AB} = I_s \cdot \left(\frac{1}{R_1} + \frac{1}{R_2}\right)^{-1}$$

Looks a lot like Ohm's Law: $V = I \cdot R$

Hmm...

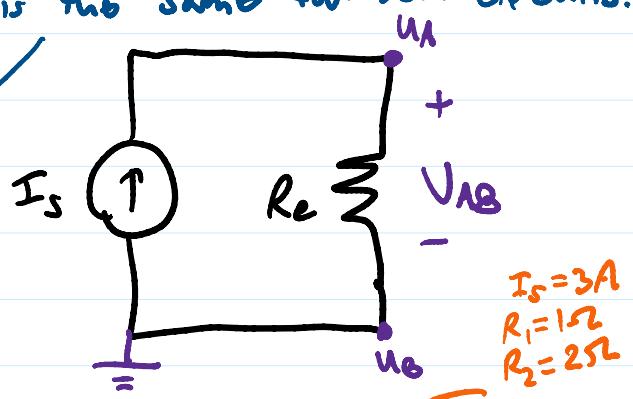Can we pick R_e so that V_{AB} is the same for both circuits?




$$R_o = \left(\frac{1}{R_1} + \frac{1}{R_2}\right)^{-1} = \left(\frac{1}{1} + \frac{1}{2}\right)^{-1} = \frac{2}{3}\Omega$$

$$V_{AB} = I_s \cdot R_o = (3A) \cdot \left(\frac{2}{3}\Omega\right) = 2V$$


Same as before!

In this example, R_1 and R_2 are connected in "parallel."


(share same voltage)

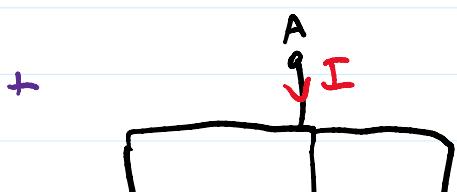

Equivalent

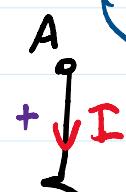

$\underline{V} \quad \underline{I}$

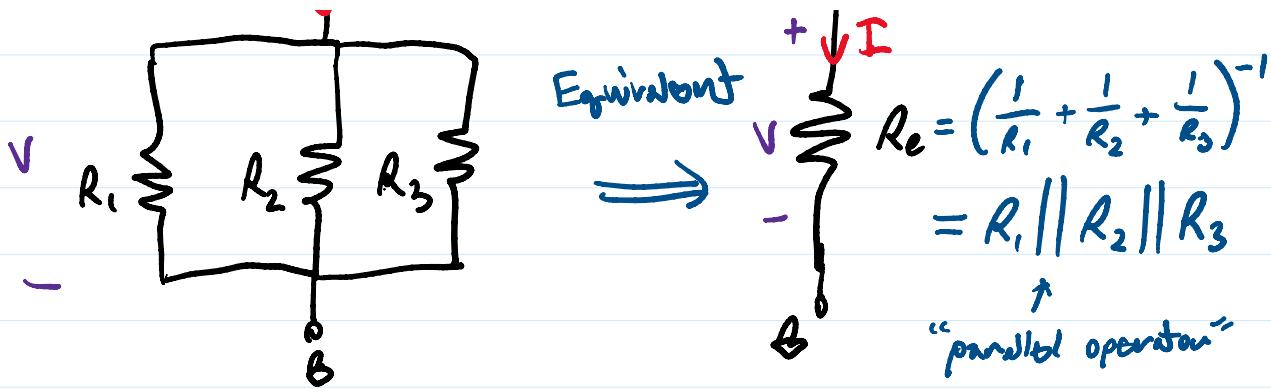


What information do we lose by making this substitution?
Current through each resistor

For the two resistor case:

$$\left(\frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \frac{R_1 R_2}{R_1 + R_2}$$

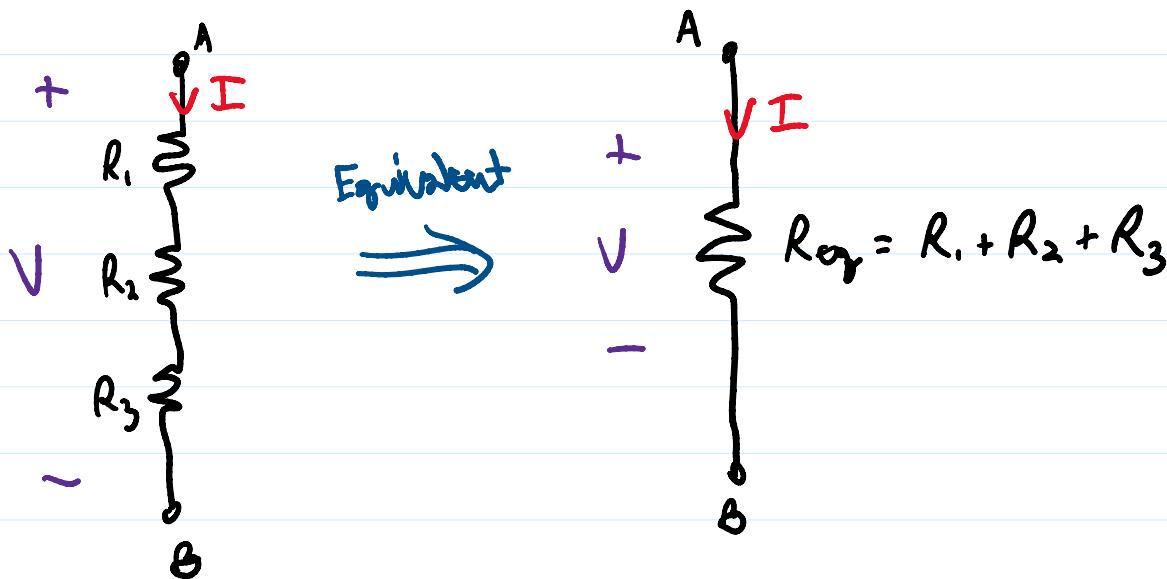
Series Resistances \leftarrow share the same current



Thévenin and Norton Equivalent Circuits:


Let us determine a reduced equivalent circuit for larger circuits with resistors + voltage + current sources

known circuit T want to know what's

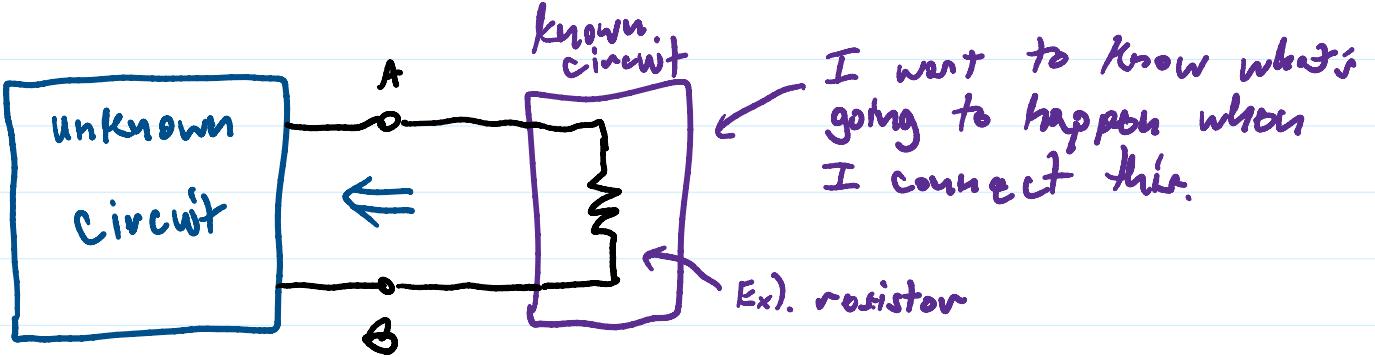

Can we determine how this unknown circuit behaves at the port AB without knowing what's inside?

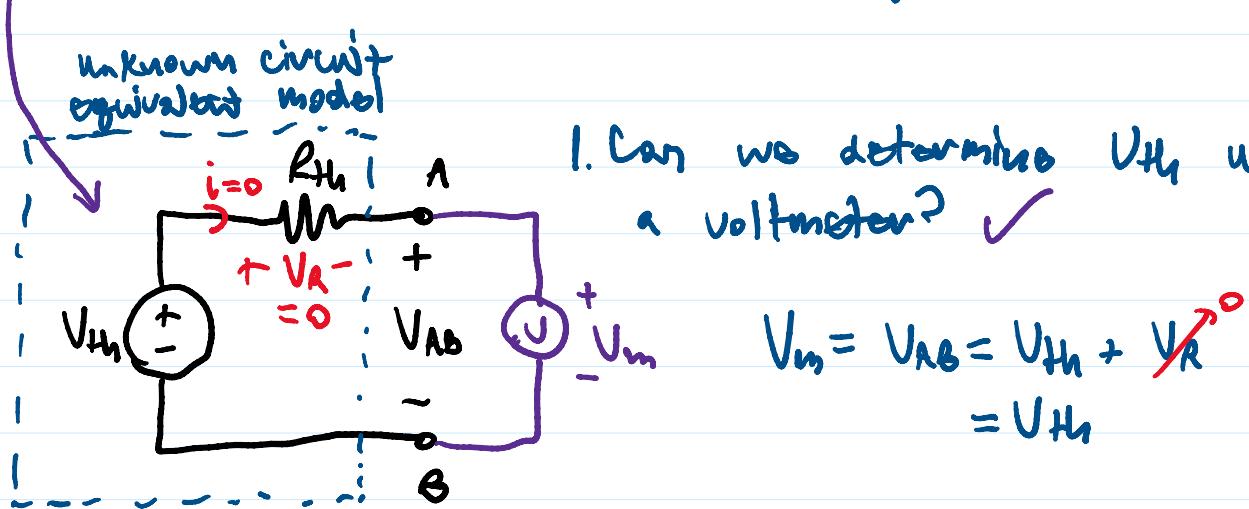Assume unknown circuit is equivalently modeled with this circuit called a **Thévenin equivalent circuit**.




1. Can we determine V_{th} using a voltmeter? ✓

* Open-circuit Test:

Measure the voltage between nodes A and B when connecting an external open circuit. $V_{AB,oc} = V_{th}$
Thévenin Voltage

2. Can we determine R_{th} as well? ✓



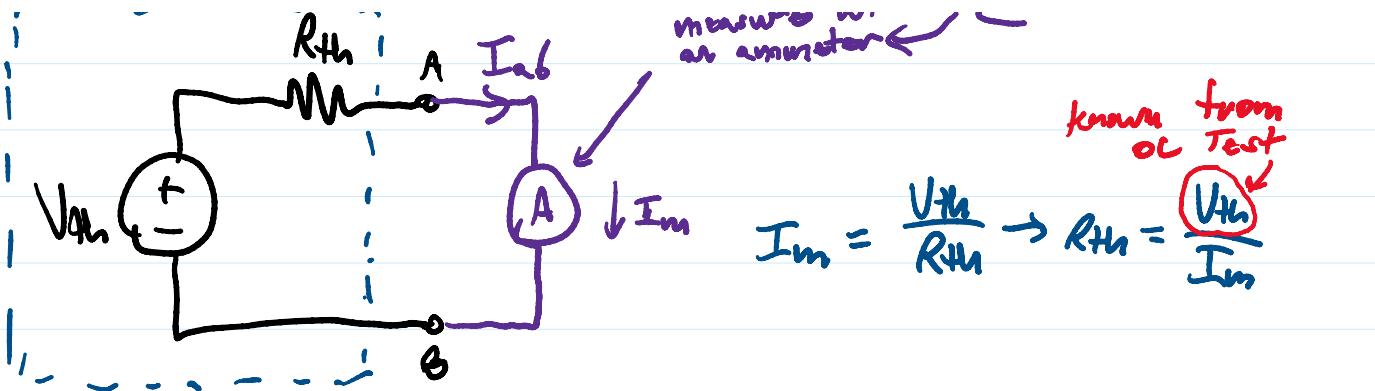


* Short-circuit Test:

Measure the current between nodes A and B when connecting an external short circuit. $I_m = \frac{V_{th}}{R_{th}} = I_{no}$


Thevenin resistance

Norton current


Consider the earlier circuit:


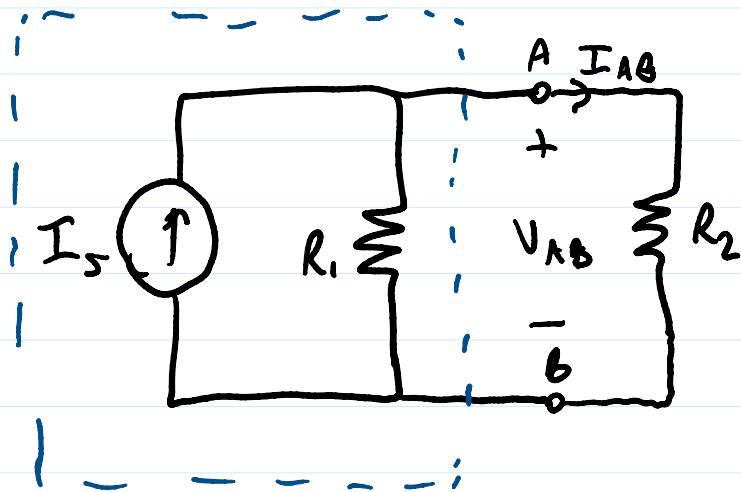


Open-circuit test:
(measure V_{AB})

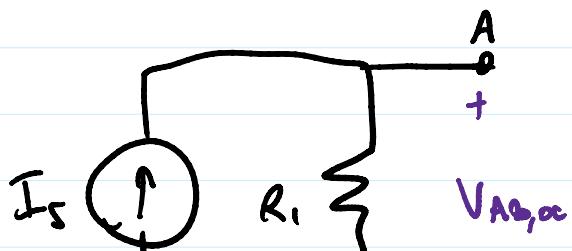

Short-circuit test:
(measure I_{AB})

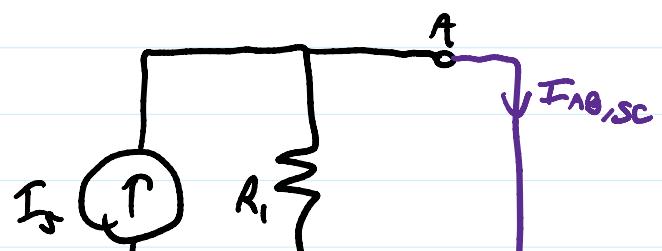

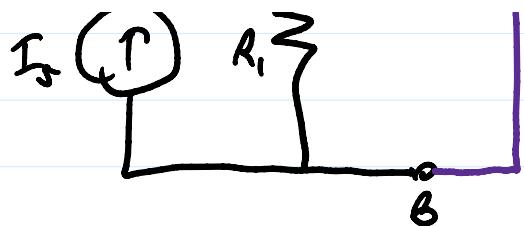
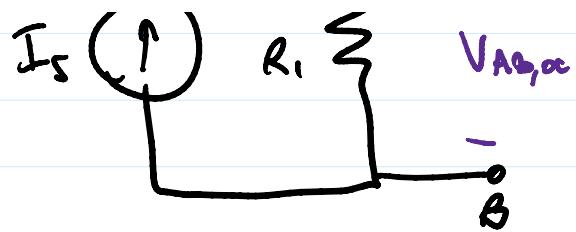


$$V_{AB} = V_{A,B,\infty} = I_s \cdot R_1$$

$$I_{no} = I_{AB,sc} = I_s$$

$$R_{th} = \frac{V_{AB}}{I_{no}} = \frac{I_s R_1}{I_s} = R_1$$

Result

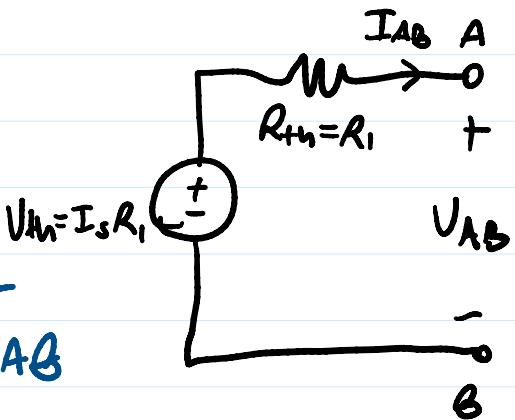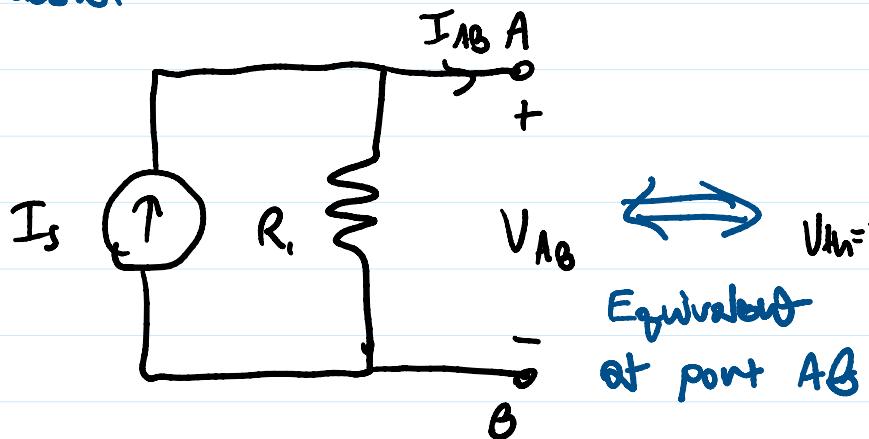

Thevenin equivalent circuit:

Norton equivalent circuit:
($R_{no} = R_{th}$)

