

## Lecture 4D: (7/13/23)


### Announcements:

- Quest Redo is available! Due Sunday night
- Lab - First Buffer Lab ← come if you've missed or not finished a lab so far
  - Touch 1 and 2 pre-labs on Ed
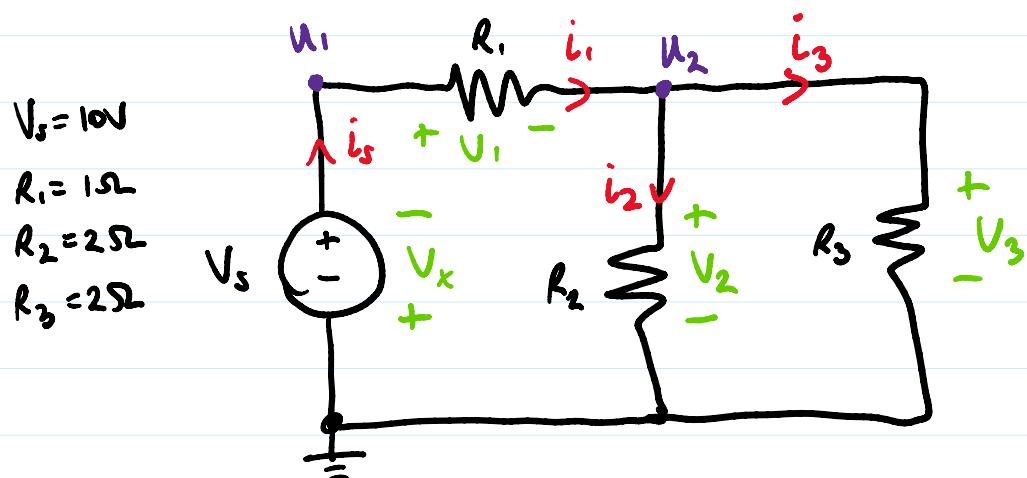
### - Today's Topics:

- Review of NVA
- Physical Resistor (Note 12)
- Power (Note 13)

Circuit from yesterday's lecture: Let's finish solving!



$$\text{At node } U_1: i_1 - \frac{U_1 - U_2}{R_1} = 0 \quad \textcircled{1}$$

$$\text{At node } u_1: i_s - \frac{u_1 - u_2}{R_1} = 0 \quad \textcircled{1}$$

$$\text{At node } u_2: \frac{u_1 - u_2}{R_1} - \frac{u_2}{R_2} - \frac{u_2}{R_3} = 0 \quad \textcircled{2}$$

$$u_1 = V_s \quad \textcircled{3}$$

Matrix vector form:  $A\vec{x} = \vec{b} \rightarrow \vec{x} = A^{-1}\vec{b}$

$$\begin{array}{l} \textcircled{1} \\ \textcircled{2} \\ \textcircled{3} \end{array} \left[ \begin{array}{ccc} -\frac{1}{R_1} & \frac{1}{R_1} & 1 \\ \frac{1}{R_1} & -\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right) & 0 \\ 1 & 0 & 0 \end{array} \right] \left[ \begin{array}{c} u_1 \\ u_2 \\ i_s \end{array} \right] = \left[ \begin{array}{c} 0 \\ 0 \\ V_s \end{array} \right]$$

Solving using substitution instead:

$$\textcircled{3} \rightarrow \textcircled{2} \quad \frac{V_s - u_2}{R_1} - \frac{u_2}{R_2} - \frac{u_2}{R_3} = 0$$

$$\cancel{R_1 R_2 R_3} \cdot \frac{(V_s - u_2)}{\cancel{R_1}} - \cancel{R_1 R_2 R_3} \frac{u_2}{\cancel{R_2}} - \cancel{R_1 R_2 R_3} \frac{u_2}{\cancel{R_3}} = 0$$

$$R_2 R_3 \cdot V_s = (R_2 R_3 + R_1 R_3 + R_1 R_2) \cdot u_2$$

$$\boxed{\begin{array}{l} V_s = 10V \\ R_1 = 1\Omega \\ R_2 = 2\Omega \\ R_3 = 2\Omega \end{array}}$$

$$u_2 = \frac{R_2 R_3}{(R_2 R_3 + R_1 R_3 + R_1 R_2)} V_s$$


$$= \frac{(2) \cdot (2)}{(2 \cdot 2 + 1 \cdot 2 + 1 \cdot 2)} \cdot (10V) = \frac{4}{8} 10V$$

$$\boxed{\begin{array}{l} u_2 = 5V \\ u_1 = 10V \end{array}}$$

We've solved the circuit!

$$U_1 = 10V$$

Check Results:

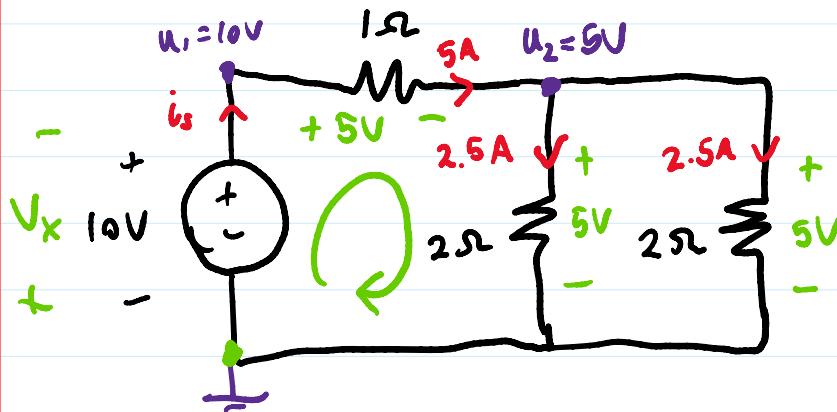

$$V = iR \rightarrow i = \frac{V}{R}$$

check KCL:

$$\textcircled{1} \quad U_2: 5A = 2.5A + 2.5A$$

check KVL:

$$+10V - 5V - 5V = 0$$




We are working towards a resistive touchscreen

- 1) Physics of Materials
- 2) Measurement


Touch Lab

Physical Resistors:

Strip:

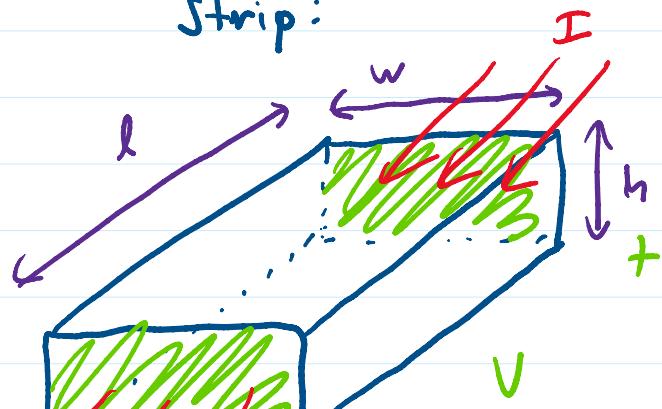

Wire:

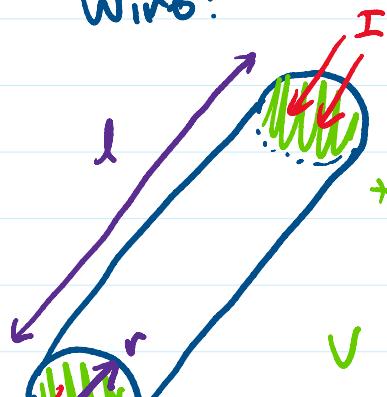



$$R = \rho \frac{l}{wh} \leftarrow R = \rho \cdot \frac{l}{A} \quad \begin{matrix} \text{length} \\ \text{(in direction of current flow)} \end{matrix} \rightarrow R = \rho \cdot \frac{l}{\pi r^2}$$

resistivity

(cross-sectional area perpendicular to current flow)


$$[\Omega] = [\Omega \cdot m] \cdot \frac{[m]}{[m^2]}$$

What is resistivity?

- Intrinsic material property
- Variable "ρ" (Greek Letter "rho")
- $\rho = \frac{1}{\sigma}$  conductivity (Greek Letter "sigma")
- More conductive  $\leftrightarrow$  less resistive
- More resistive  $\leftrightarrow$  less conductive

[https://en.wikipedia.org/wiki/Electrical\\_resistivity\\_and\\_conductivity](https://en.wikipedia.org/wiki/Electrical_resistivity_and_conductivity)


Another Strip...

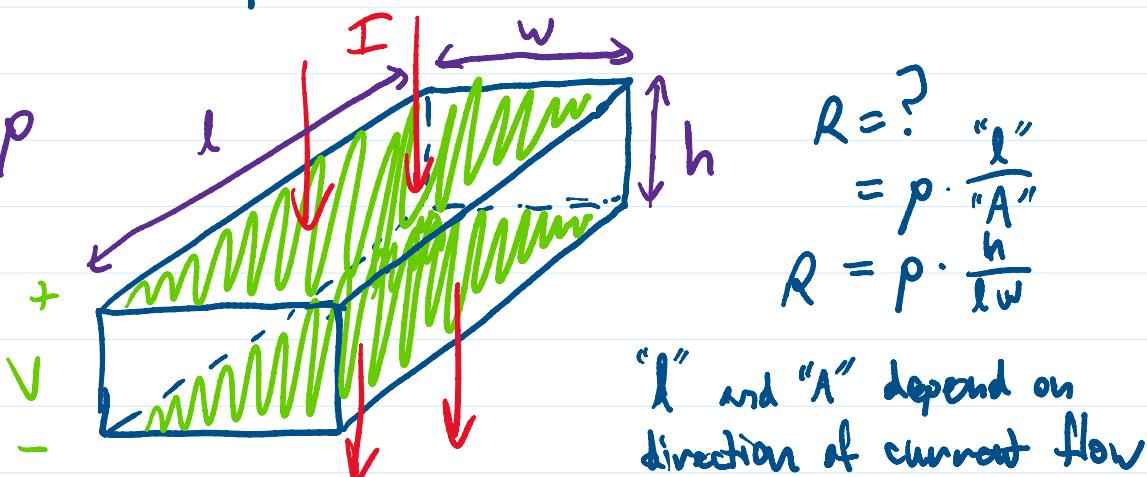



$\rho$  and  $A$  depend on direction of current flow


## Demo with wooden blocks

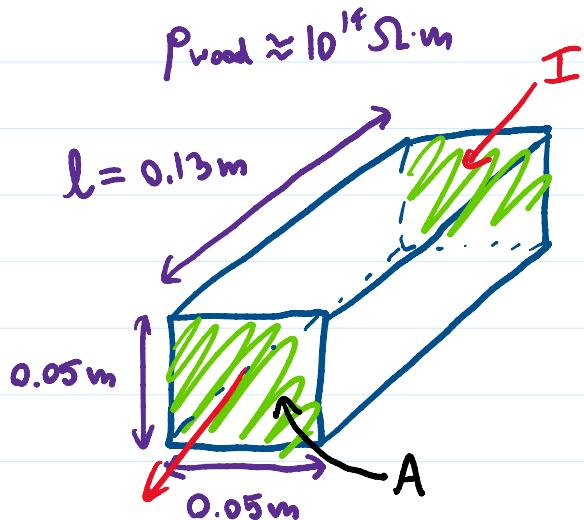

$$R = \rho \frac{l}{A} = (10^{14} \Omega \cdot \text{m}) \cdot \frac{(0.13 \text{ m})}{(0.0025 \text{ m}^2)} = 5.2 \cdot 10^{15} \Omega$$


Back-to-back?
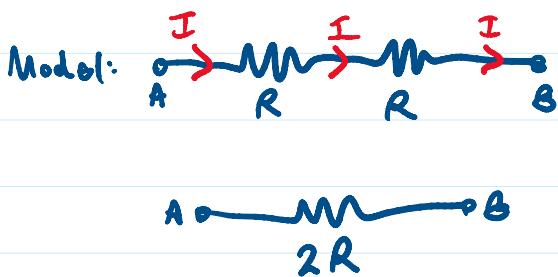
$$R_{\text{tot}} = \rho \frac{(2l)}{A} = 2R$$



Side-to-side?
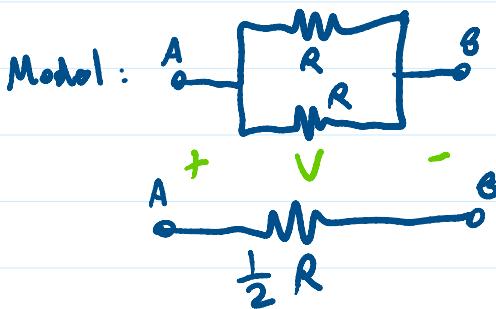
$$R_{\text{tot}} = \rho \frac{l}{(2A)} = \frac{1}{2} R$$



"series"-connected  
(share the same current)


"parallel"-connected  
(share the same voltage)

NVA Review:

Find the node voltages

Ex). Voltage Divider

## Ex.). Voltage Divider

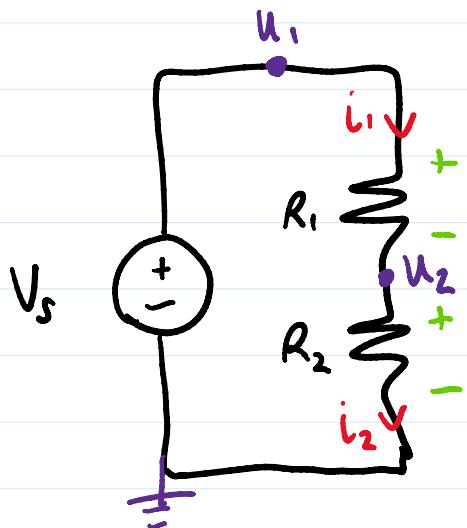

$$U_1 = V_s$$

$$U_2 = \frac{R_2}{R_1 + R_2} \cdot V_s$$

- Step 1: Label reference node  
 Step 2: Label unknown node voltages  
 Step 3: Label currents key unknowns  
 Step 4: Add +/- labels  
 Step 5: Identify unknowns (U\_1, U\_2, i\_1, i\_2)  
 Step 6a: KCL equations at unknown nodes

$$U_1 = V_s \quad U_2 = ? \rightarrow i_1 - i_2 = 0$$

known ↑

Step 6b: I/V characteristics

$$U_1 - U_2 = i_1 R_1, \quad U_2 - 0 = i_2 R_2$$


Step 7: Substitute and solve

$$i_1 - i_2 = 0 \rightarrow \frac{U_1 - U_2}{R_1} - \frac{U_2}{R_2} = 0$$

Solve equations:

$$U_1 = V_s$$
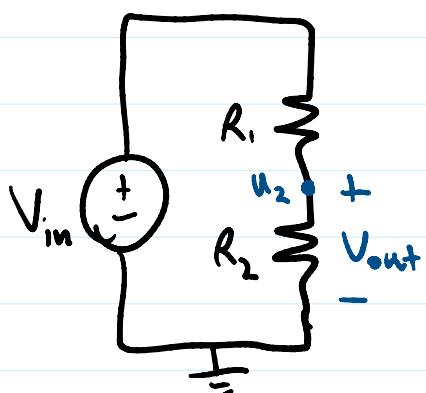
$$\frac{U_1 - U_2}{R_1} - \frac{U_2}{R_2} = 0 \rightarrow \frac{V_s}{R_1} - \frac{1}{R_1} U_2 - \frac{1}{R_2} U_2 = 0 \quad \text{Multiply by } R_1 \text{ and } R_2$$



$$V_s \cdot R_2 - R_2 U_2 - R_1 U_2 = 0$$

$$U_2 \cdot (R_1 + R_2) = R_2 \cdot V_s$$

$$U_2 = \frac{R_2}{R_1 + R_2} \cdot V_s$$

0 < x < 1

Why is it called a voltage divider?

Pick:  $R_1 = 1\Omega$ ,  $R_2 = 3\Omega$

$\downarrow R_2$

Pick:  $R_1 = 1\Omega$ ,  $R_2 = 3\Omega$

$$V_{out} = \frac{R_2}{R_1 + R_2} \cdot V_{in} = \frac{3}{1+3} \cdot V_{in} = \frac{3}{4} \cdot V_{in}$$

total series resistance

## Power.

Electricity performs two basic functions:

- 1) Transfer information
- \* 2) Transfer energy

It's really hard to store electrical energy

What is power?  $P = \frac{\partial E}{\partial t}$  ← flow of energy  
watt [W] =  $\frac{[J]}{[s]}$  joule second

Electrical power:

$$P = V \cdot i = \frac{\partial E}{\partial q} \cdot \frac{\partial q}{\partial t} = \frac{\partial E}{\partial t} \checkmark$$

↑  
ALWAYS TRUE

$V$   $i$

(passive sign convention)


$\left\{ \begin{array}{l} P > 0 \rightarrow \text{dissipates power} \\ P < 0 \rightarrow \text{delivers power} \end{array} \right.$

Let's consider our voltage divider example again

$$V = iR$$

$$\frac{U_1 = 4V}{i} \quad , 1A$$
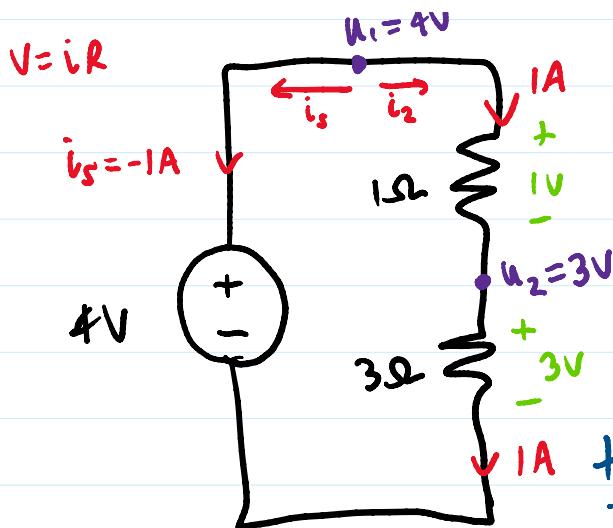
$$V_S = 4V, R_1 = 1\Omega, R_2 = 3\Omega$$



$$V_S = 4V, R_1 = 1\Omega, R_2 = 3\Omega$$

$$U_2 = \frac{R_2}{R_1 + R_2} V_S = \frac{3\Omega}{1\Omega + 3\Omega} \cdot 4V = 3V$$

$$P_S = V_S \cdot i_s = (4V) \cdot (-1A) = -4W$$

$$P_{1\Omega} = (1V) \cdot (1A) = +1W$$

$$P_{3\Omega} = (3V) (1A) = +3W$$

Conservation of energy/power:

$$P_{\text{total}} = 0W$$